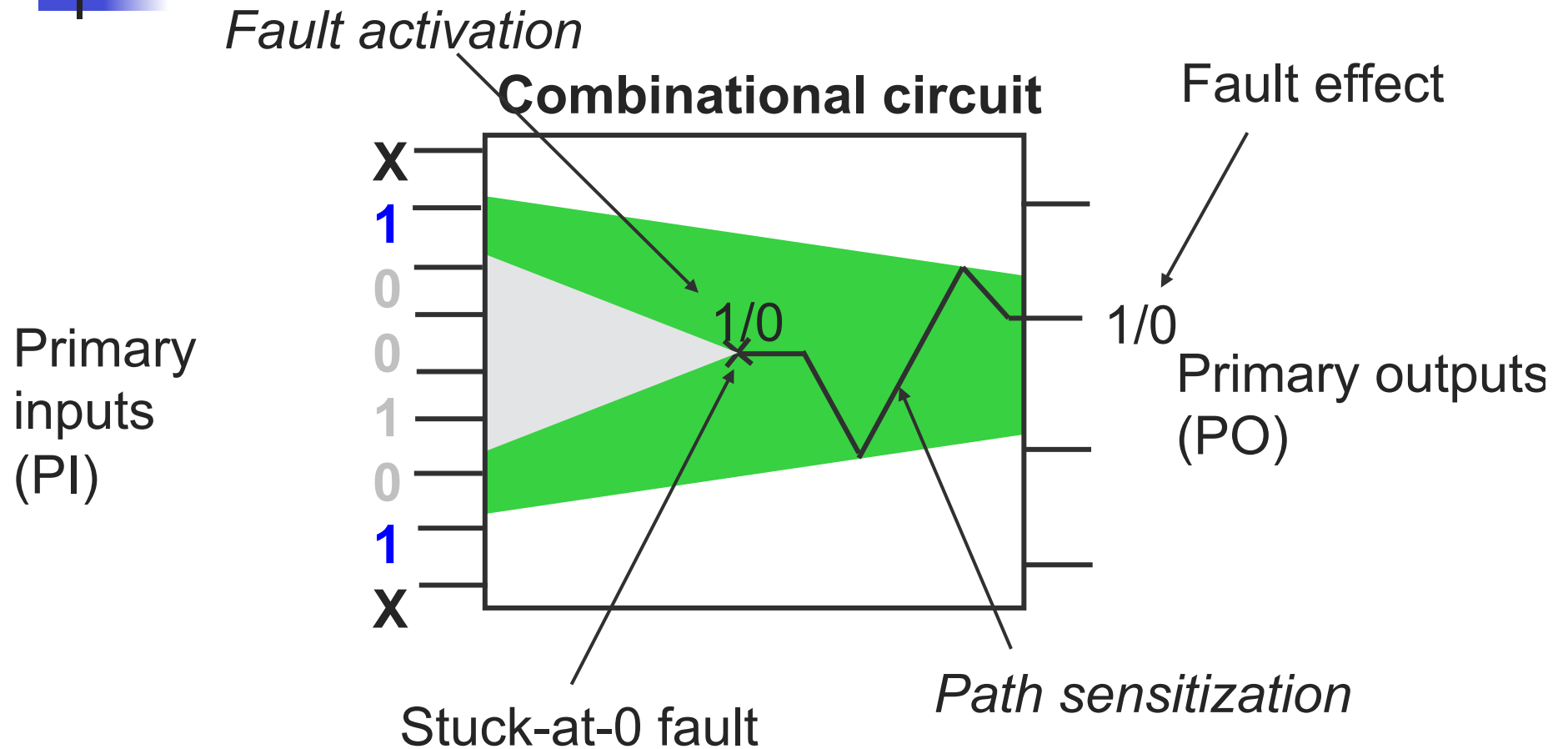


# ATPG and Fault Simulation


Alberto Bosio

[bosio@lirmm.fr](mailto:bosio@lirmm.fr)

# What is a test?




# What is a test?

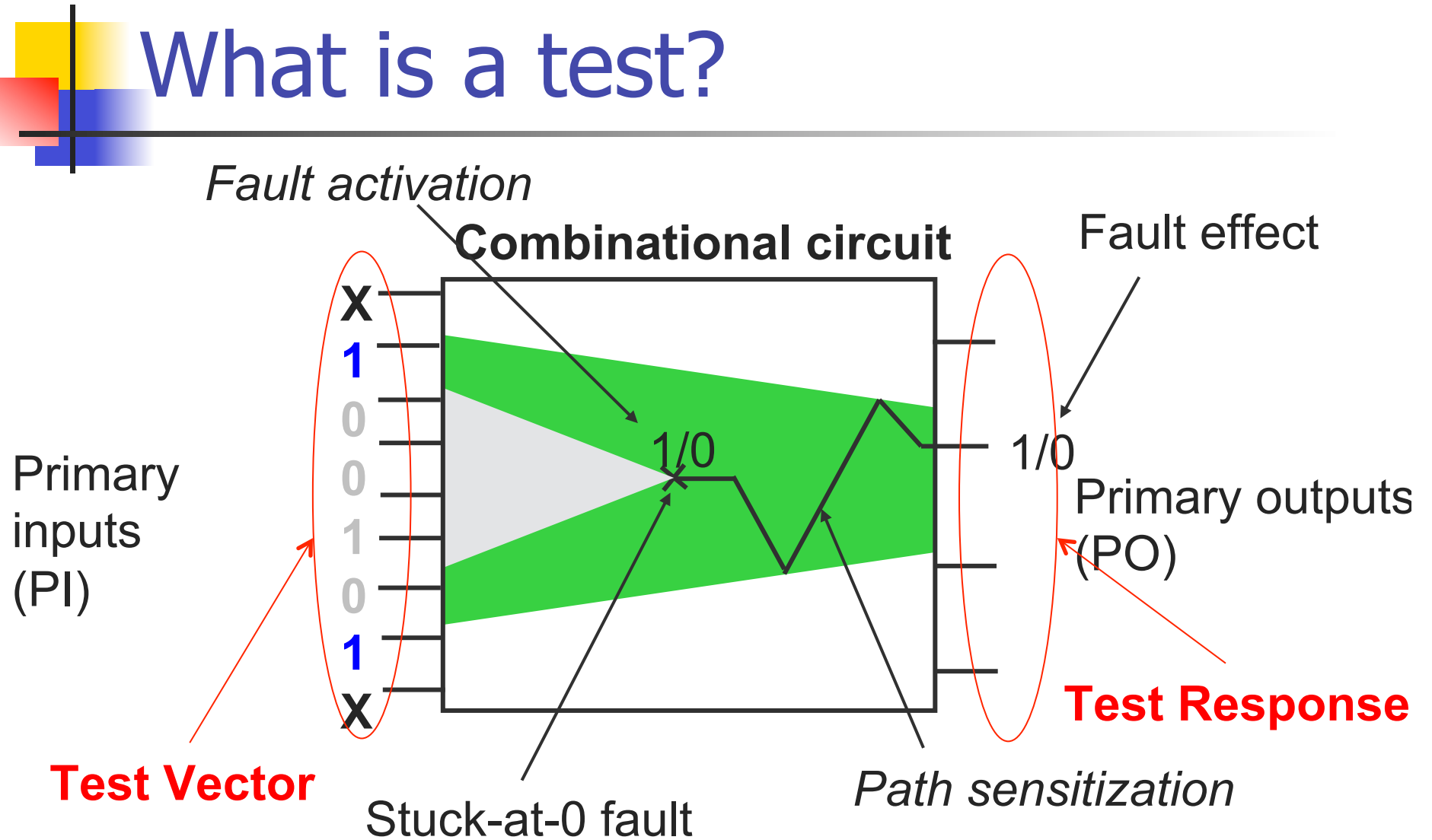


# Example

- Generate a test for **e stuck-at-1**

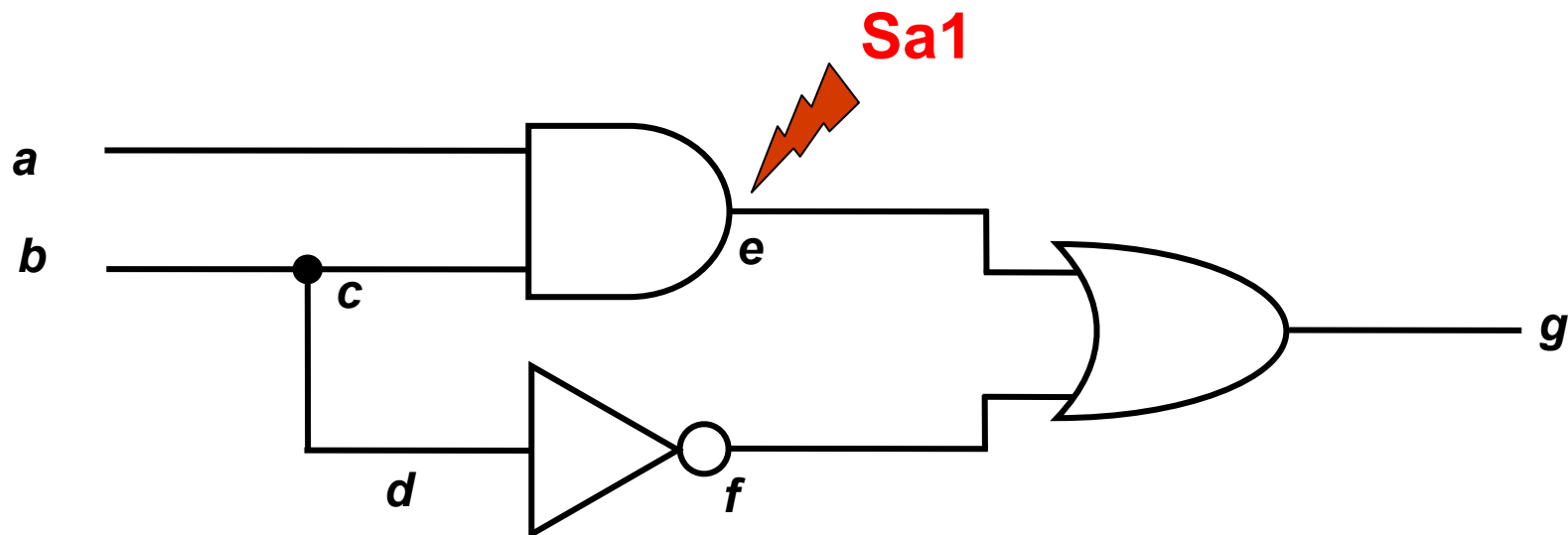


# Example

- 1) Activate the fault

 


# Example

- 1) Activate the fault

 


# Example

- 1) Activate the fault

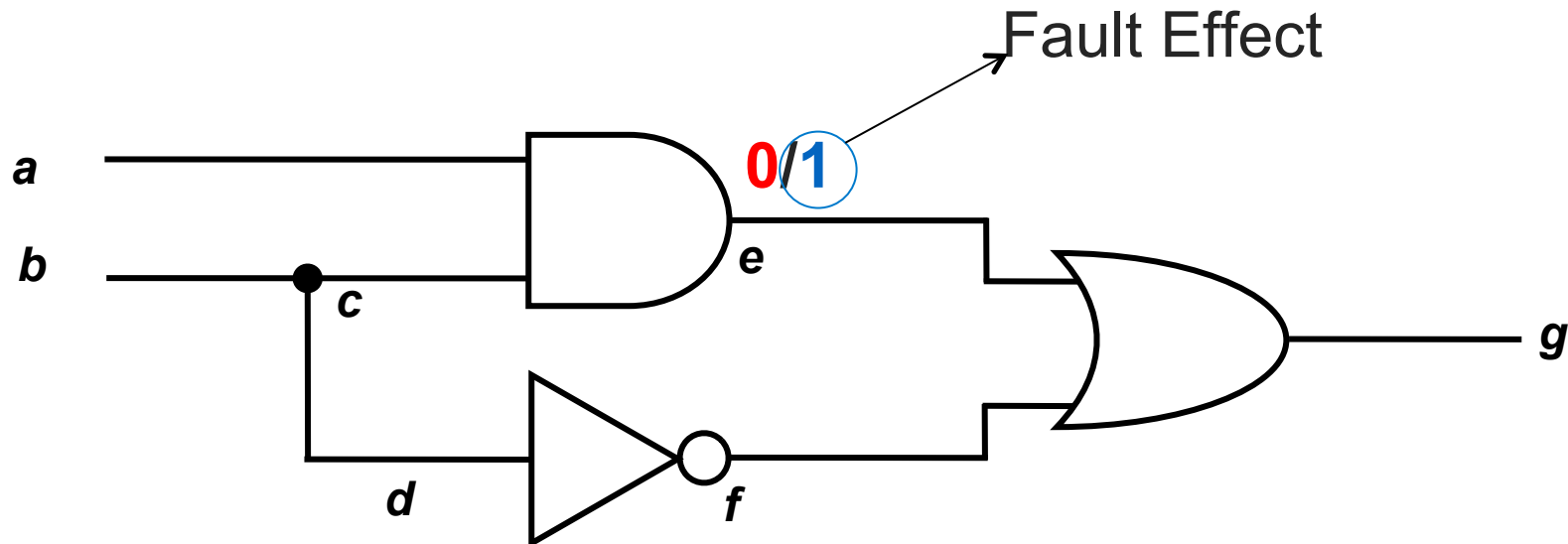

# Example


- 1) Propagate the fault effect

 




# Example

- 1) Propagate the fault effect

 


# Example

- 1) Propagate the fault effect

 


# Example

- 1) Propagate the fault effect

 


# Example

- Justification

 


# Example

- Justification

 

# Example

- Justification

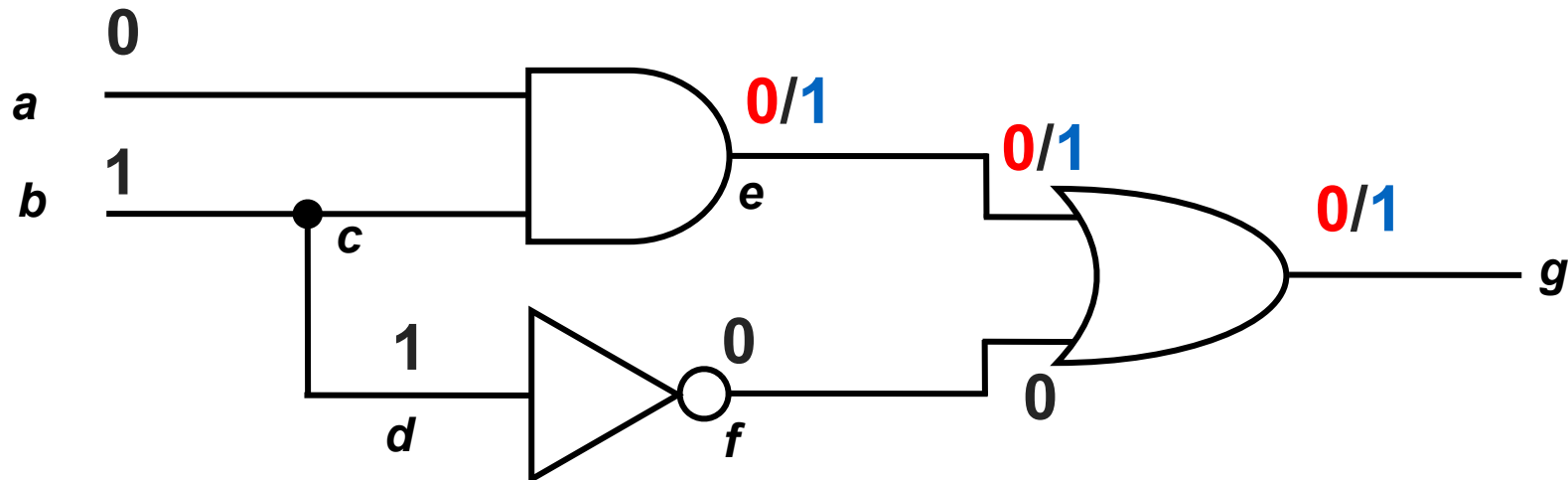




# Some Considerations

---

- Test is easy
- But....

# Some problems (the complexity)
 
## Intel® Core™ i7-3960X Processor Die Detail




2.2 Billion Transistors




# Some problems (the circuit)

- Generate a test for **c stuck-at-1**

 
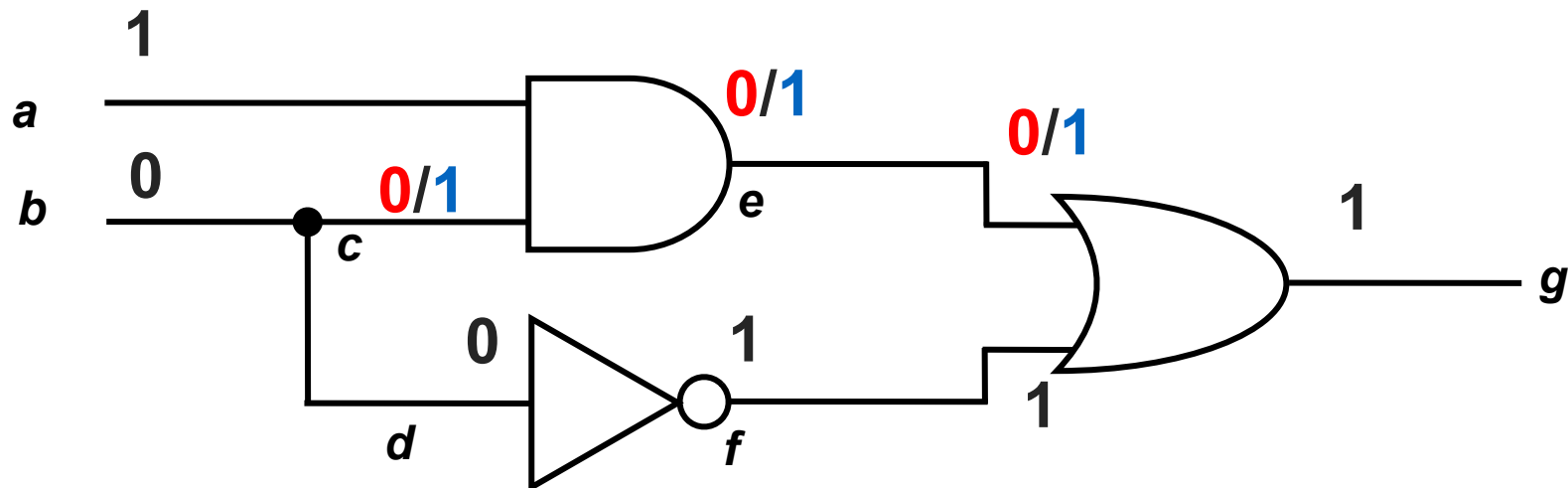
# Some problems (the circuit)

- **c stuck-at-1** is an untestable fault






# Goals

---

- You must use the appropriate tool
  - Automatic Test Pattern Generator (ATPG)

# ATPG Architecture

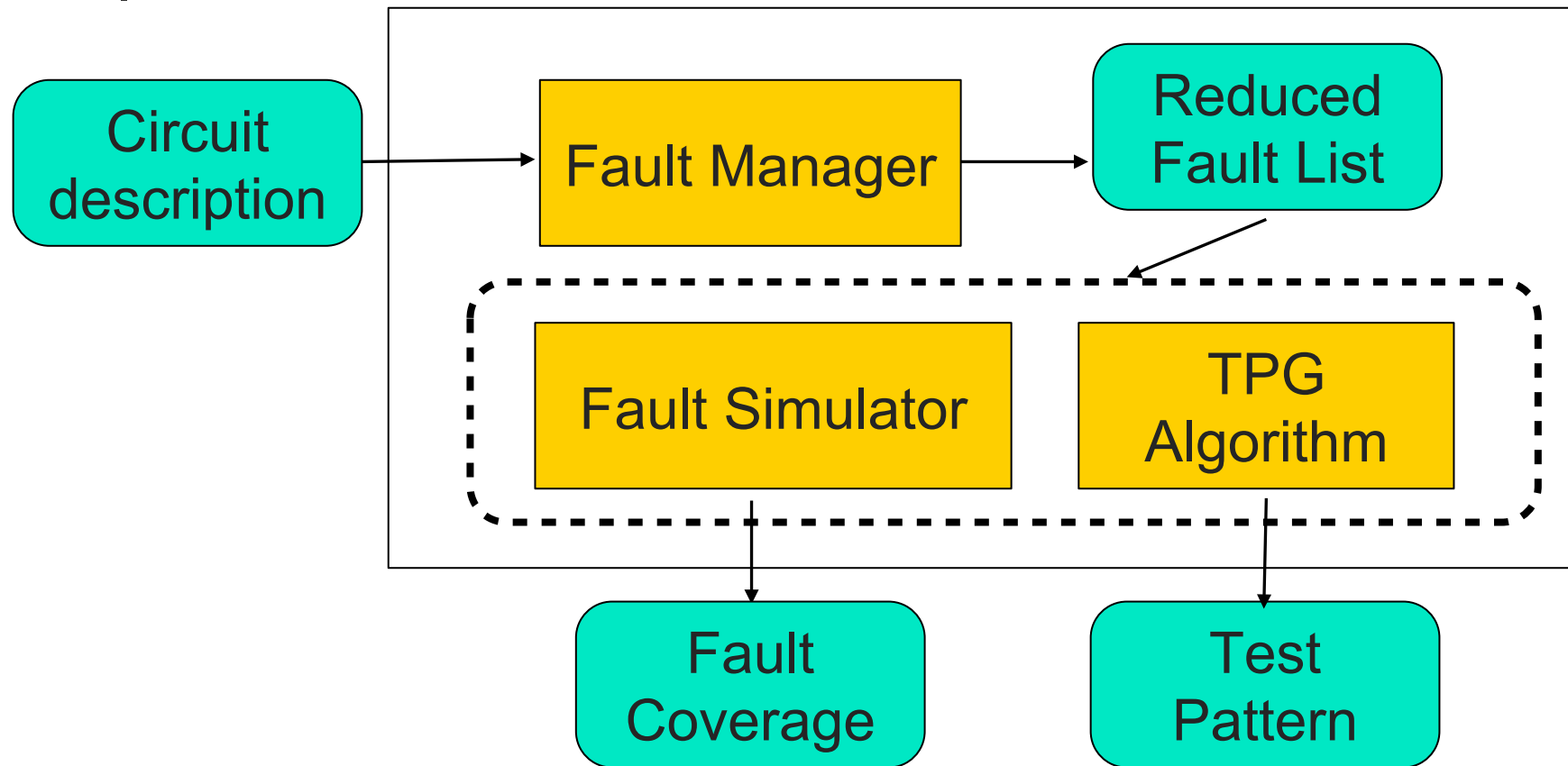

# ATPG Architecture

**Fault Coverage (FC) = # Detected Faults/#Total Faults**

Fault  
Coverage

Test  
Pattern




# The test plan

---

- Step 1:
  - Identify the set of target faults (**complete fault list**).
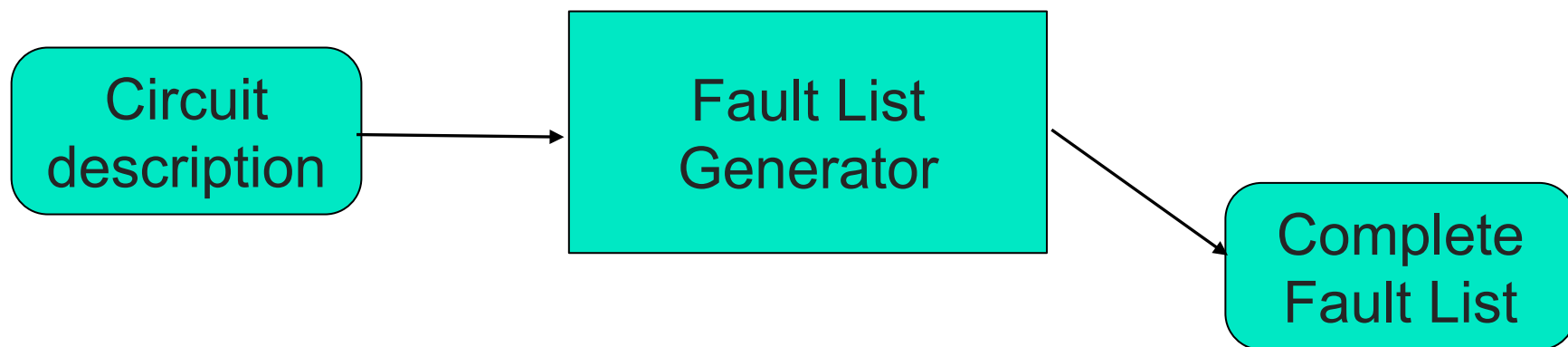
# The test plan

- Step 1:
  - Tools – Fault list generator
    - (One of the components of the Fault Manager).





# The test plan (cont'd)

---

- Step 1:
  - Identify the set of target faults (complete fault list).
- Step 2:
  - Identify the minimum set of distinct target faults (**fault collapsing**)






# The test plan


---

- Step 2:
  - Tools – Fault collapser (One of the components of the Fault Manager).

# Fault Manager

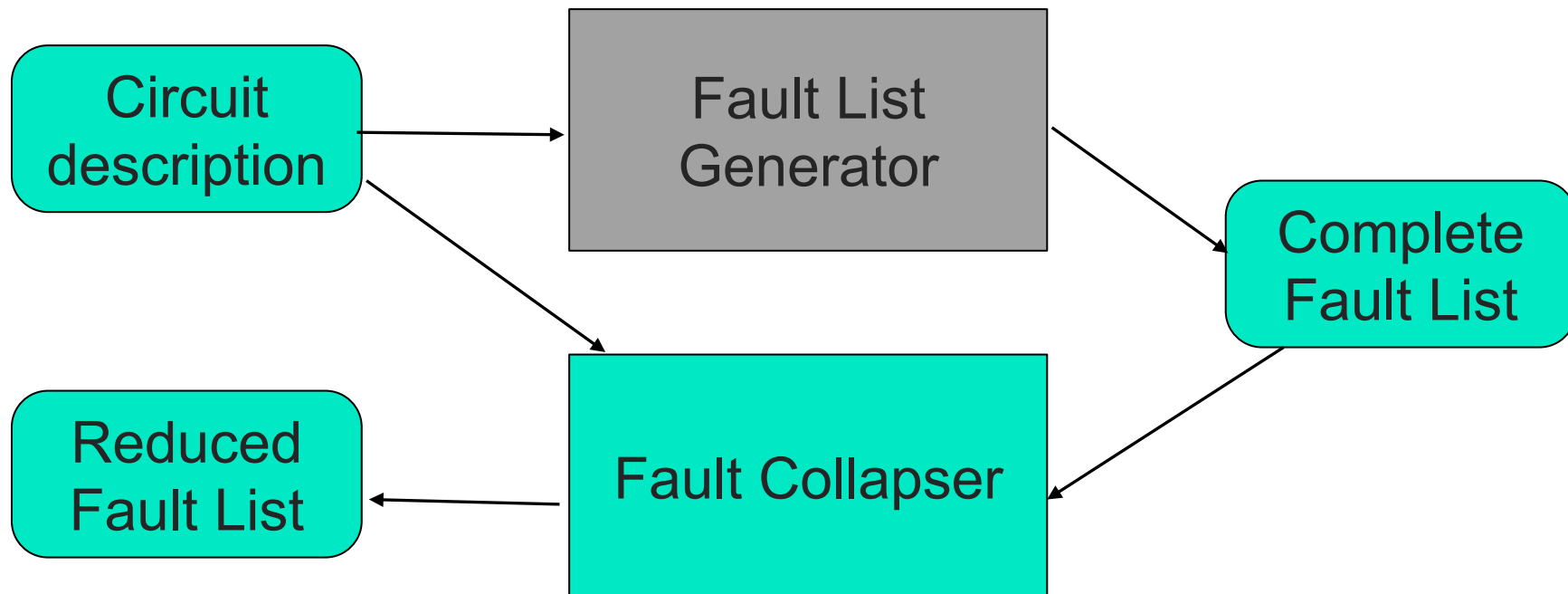

# Fault Manager

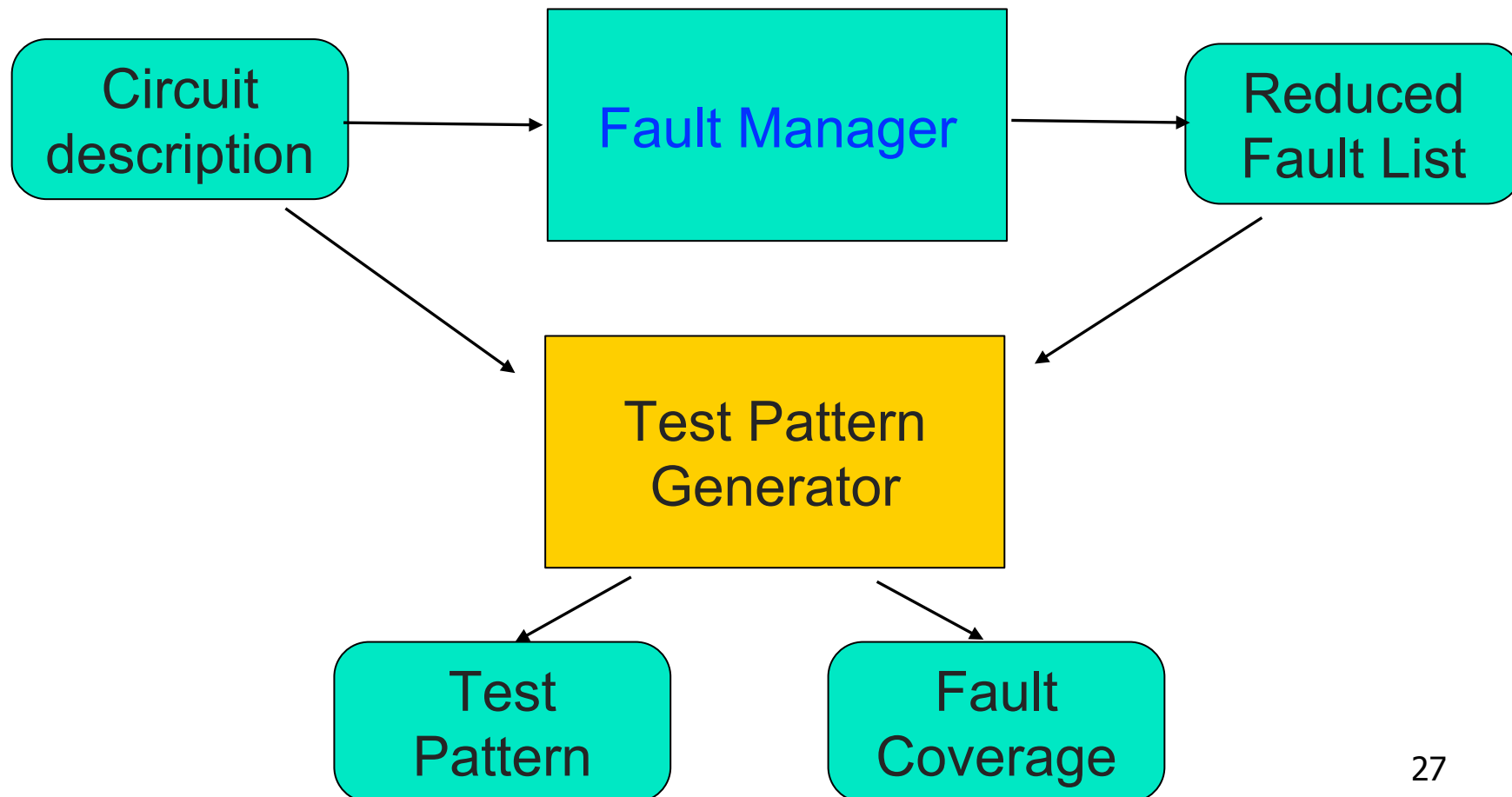



## The test plan (cont'd)

---

- Step 2:
  - Identify the minimum set of distinct target faults (fault collapsing)
- Step 3:
  - Generate, **at no charge**, an initial set of patterns (manually, from design validation, randomly, ...)



## The test plan (cont'd)

---

- Step 3:
  - Generate, at no charge, an initial set of patterns (manually, from design validation, randomly, ...)
- Step 4:
  - Update the list of detected faults (**fault simulation**)




## Step 4

---

- Tools
  - Fault Simulators: identify the set of faults covered by each test pattern.

# Fault Simulator

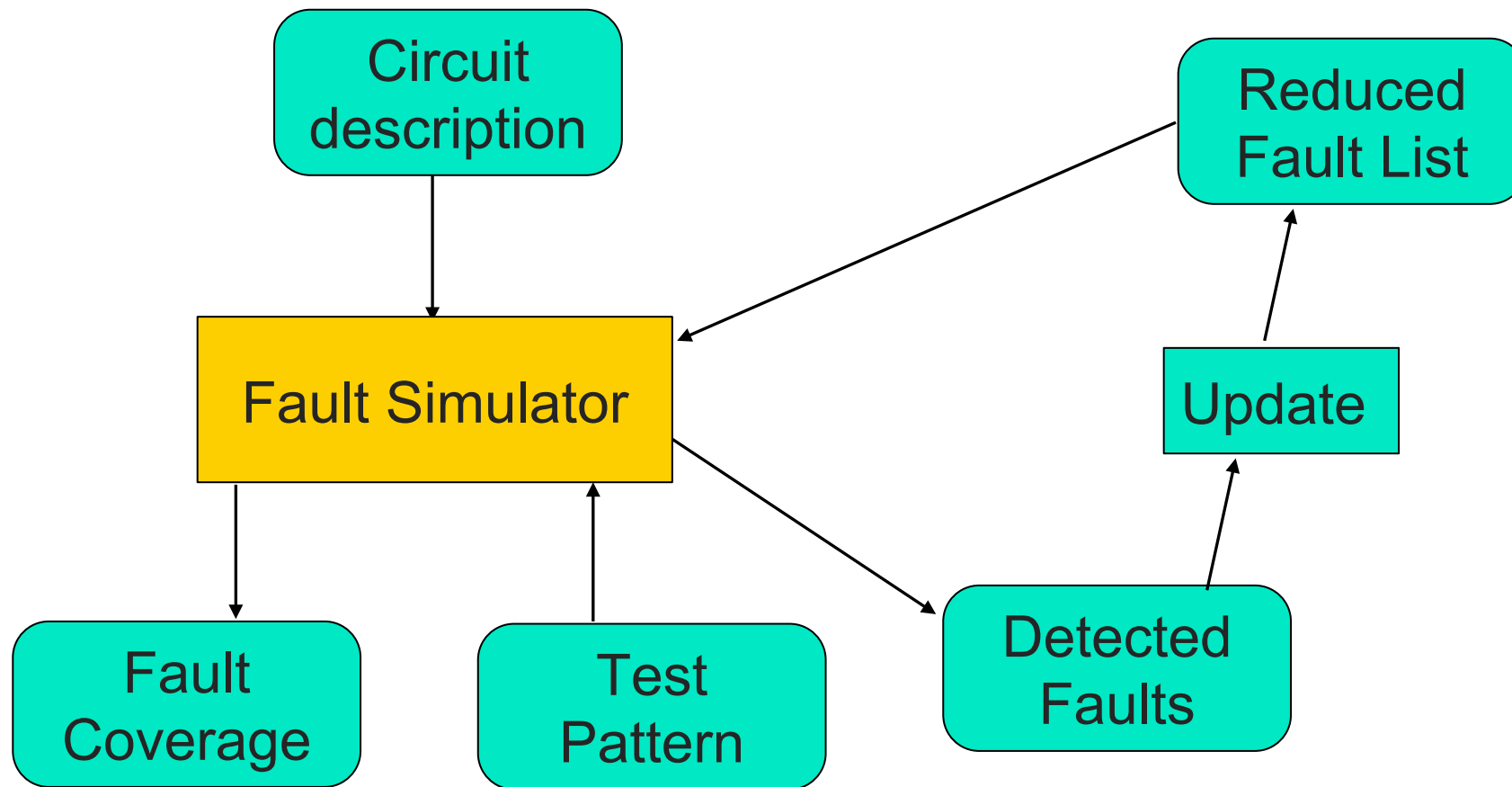



## The test plan (cont'd)

---

- Step 4:
  - Update the list of detected faults (fault simulation)
- Step 5:
  - Generate a set of patterns to cover the uncovered faults (**TPG**)







## Step 5

---

- Tools
  - ATPG: Automatic Test Pattern Generator

# TPG

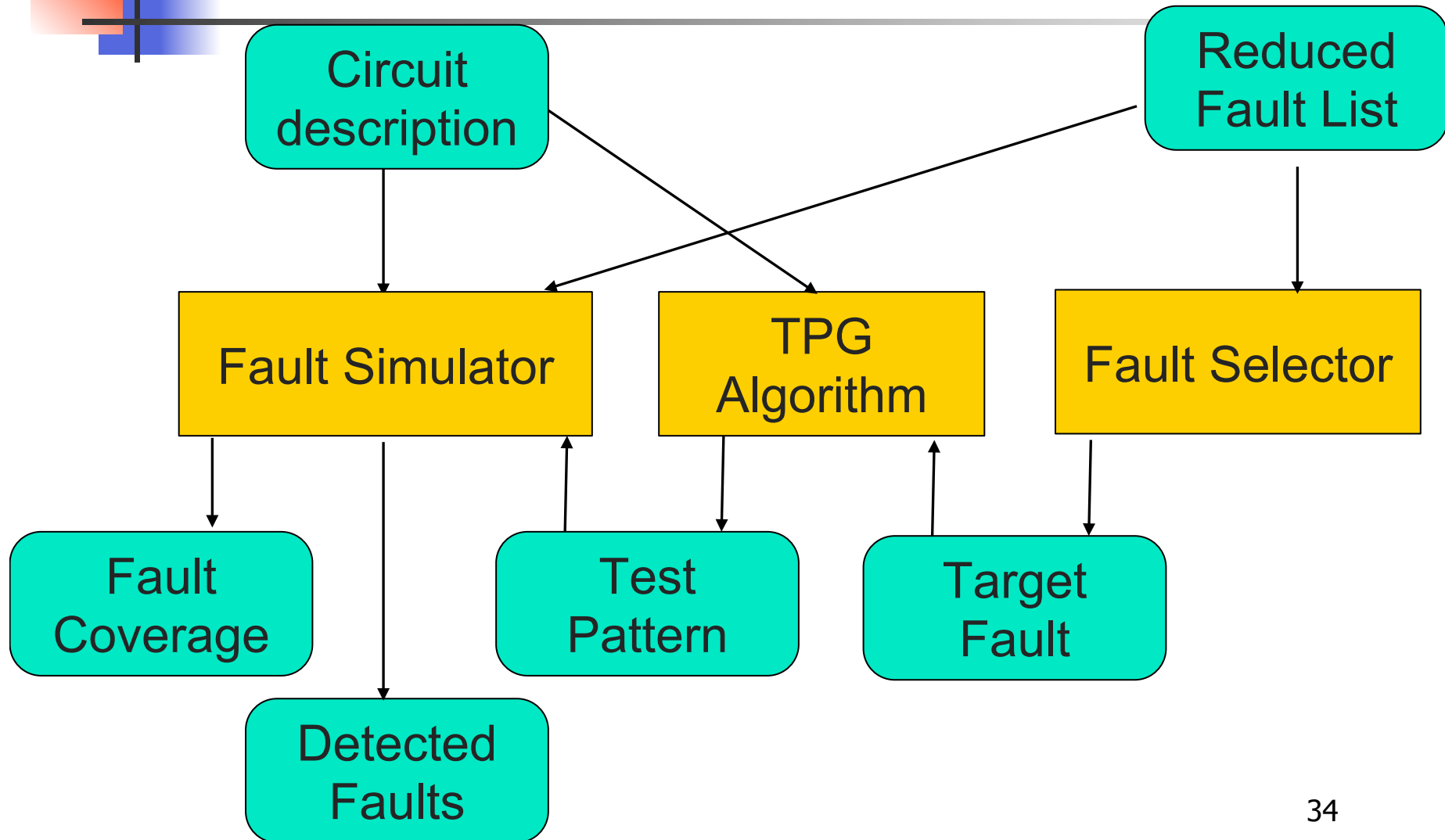

 

- 
- They cycle through three sub-phases:
    - target fault selection
    - Pattern generation
    - Covered fault list updating.



## The test plan (cont'd)

---

- Step 5:
  - Generate a set of patterns to cover the uncovered faults (TPG)
- Step 6 (optional):
  - Testability analysis
- Step 7 (optional):
  - Compact test pattern set.



## Step 6

---

- Goal

- Estimate the effort needed to test the UUT:
  - Pattern length
  - Fault coverage
  - CPU time
  - ...
  - Identify hard-to-test areas

- Tools

- Testability Analyzer
- **Experience.**



# The test plan (cont'd)

---

- Step 5:
  - Generate a set of patterns to cover the uncovered faults (TPG)
- Step 6 (optional):
  - Testability analysis
- Step 7 (optional):
  - Compact test pattern set.



# Testability Analyzer

---

- High trade-off between result accuracy and CPU time.
- A Circuit is testable when you ATPG can manage it!!!!



# Fault Simulation\*

---

- Problem and motivation
- Fault simulation algorithms
  - Serial
  - Parallel
  - Deductive

\*The lecture has been taken from Prof. Agrawal VLSI test course ([http://www.eng.auburn.edu/~agrawvd/COURSE/E7250\\_06/course.html](http://www.eng.auburn.edu/~agrawvd/COURSE/E7250_06/course.html))





# Problem and Motivation

---

- Given
  - A circuit
  - A sequence of test vectors
  - A fault model
- Determine
  - Fault coverage - fraction (or percentage) of modeled faults detected by test vectors
  - Set of undetected faults



# Problem and Motivation

---

- Motivation
  - Determine test quality and in turn product quality
  - Find undetected fault targets to improve tests




# Fault Simulation Scenario

---

- Circuit model: mixed-level
  - Mostly logic with some switch-level for high-impedance (Z) and bidirectional signals
  - High-level models (memory, etc.) with pin faults
- Signal states: logic
  - Two (0, 1) or three (0, 1, X) states for purely Boolean logic circuits
  - Four states (0, 1, X, Z) for sequential MOS circuits
- Timing:
  - Zero-delay for combinational and synchronous circuits
  - Mostly unit-delay for circuits with feedback

# Fault Simulation Scenario (Continued)

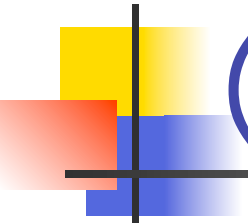

---

- Faults:
  - Mostly single stuck-at faults
  - Sometimes stuck-open, transition, and path-delay faults; analog circuit fault simulators are not yet in common use
  - Equivalence fault collapsing of single stuck-at faults
  - Fault-dropping -- a fault once detected is dropped from consideration as more vectors are simulated; fault-dropping may be suppressed for diagnosis
  - Fault sampling -- a random sample of faults is simulated when the circuit is large



# Fault Simulation Algorithms

---

- Serial
- Parallel
- Deductive
- ....



# Serial Algorithm

---

- Algorithm: Simulate fault-free circuit and save responses. Repeat following steps for each fault in the fault list:
  - Modify netlist by injecting one fault
  - Simulate modified netlist, vector by vector, comparing responses with saved responses
  - If response differs, report fault detection and suspend simulation of remaining vectors
- Advantages:
  - Easy to implement; needs only a true-value simulator, less memory
  - Most faults, including analog faults, can be simulated



# Serial Algorithm


---

- Disadvantage: Much repeated computation; CPU time prohibitive for VLSI circuits
- Alternative: Simulate many faults together



# Serial Algorithm

---

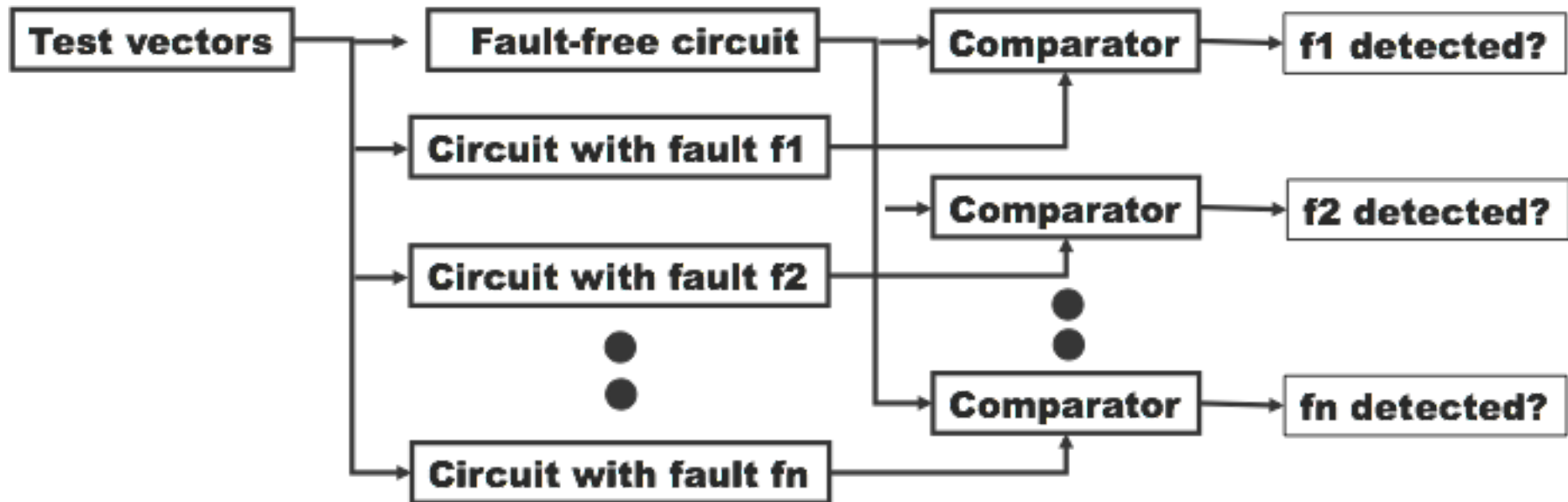





# Serial algorithm

---

- + very simple
- - not efficient
  - Intel I7 is about  $\sim 10\text{M}$  gates
  - 20M faults, 1 simulation = 1s
  - 20Ms  $\approx$  **231 days**




# Parallel Fault Simulation

---

- Compiled-code method; best with two-states (0,1)
- Exploits inherent bit-parallelism of logic operations on computer words
- Storage: one word per line for two-state simulation
- Multi-pass simulation: Each pass simulates  $w-1$  new faults, where  $w$  is the machine word length
- Speed up over serial method  $\sim w-1$
- Not suitable for circuits with timing-critical and non-Boolean logic

# Parallel Fault Simulation

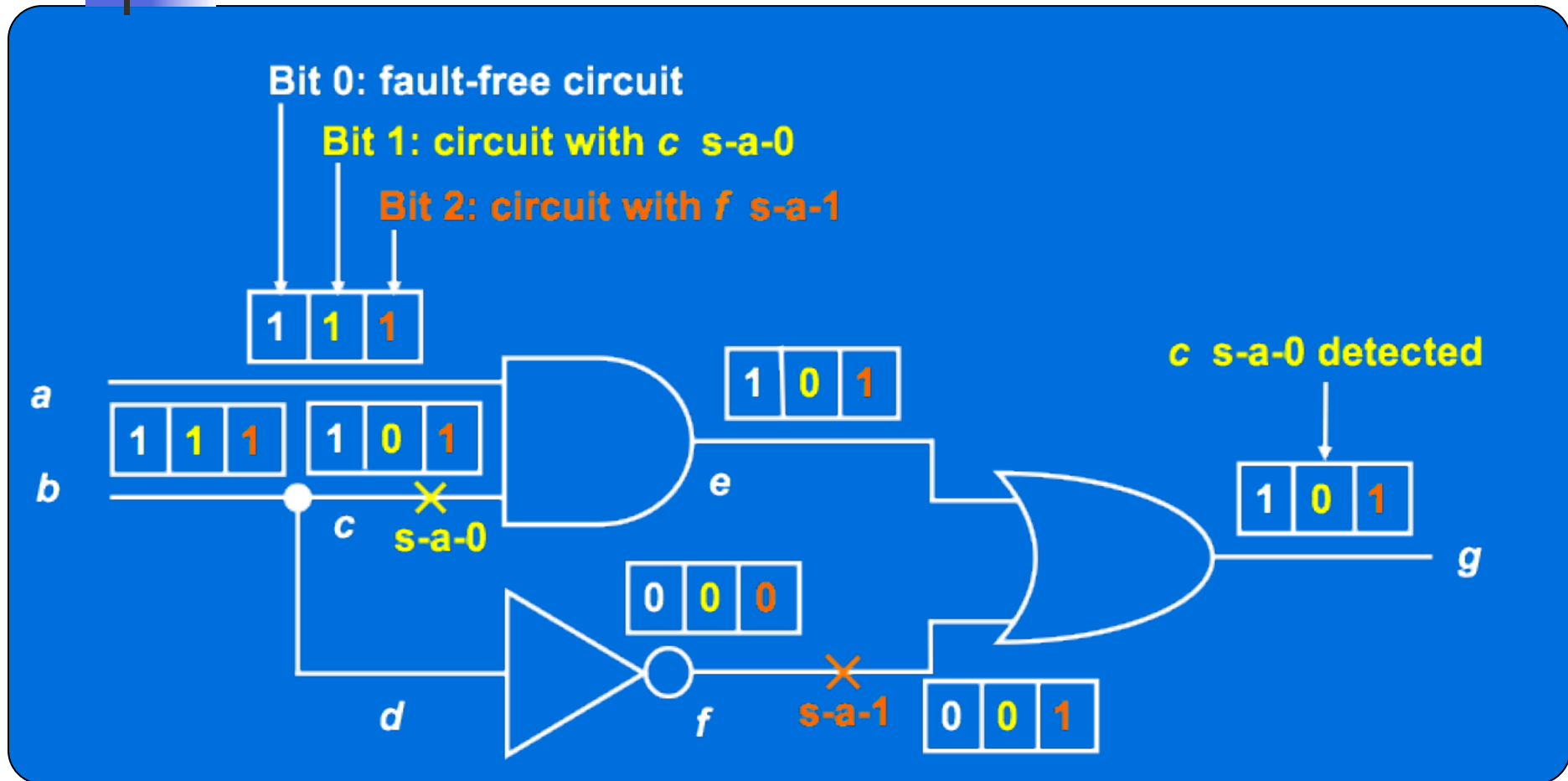



# Parallel algorithm

---

- + still very simple
- + more efficient than serial
  - Intel I7 is about  $\sim 10\text{M}$  gates
  - $20\text{M}$  faults, 1 simulation = 1s
  - $20\text{Ms} \sim = \mathbf{231 \text{ days}}$
  - Using a 64bits machine
  - $\mathbf{231/63} \sim = \mathbf{4 \text{ days}}$




# Deductive Fault Simulation

---

- One-pass simulation
- Each line  $k$  contains a list  $L_k$  of faults detectable on it
- Following true-value simulation of each vector, fault lists of all gate output lines are updated using set-theoretic rules, signal values, and gate input fault lists
- PO fault lists provide detection data
- Limitations:
  - Set-theoretic rules difficult to derive for non-Boolean gates
  - Gate delays are difficult to use
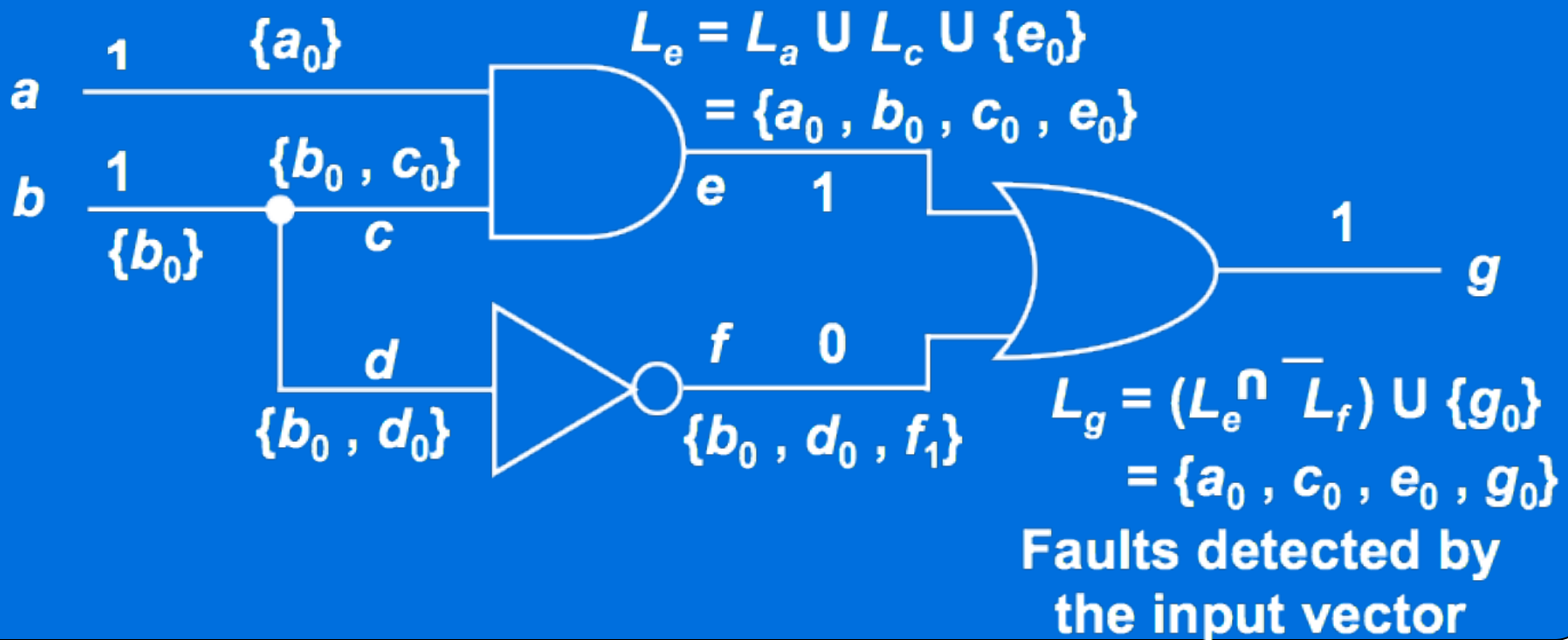
# Deductive Fault Simulation

Notation:  $L_k$  is fault list for line  $k$   
 $k_n$  is s-a-n fault on line  $k$






# Deductive algorithm

---

- - complex
- ++ more efficient than parallel
  - Intel I7 is about  $\sim 10\text{M}$  gates
  - 20M faults, 1 simulation = 1s
  - $20\text{Ms} \sim \underline{\mathbf{1s}}$
- - it requires a lot of memory
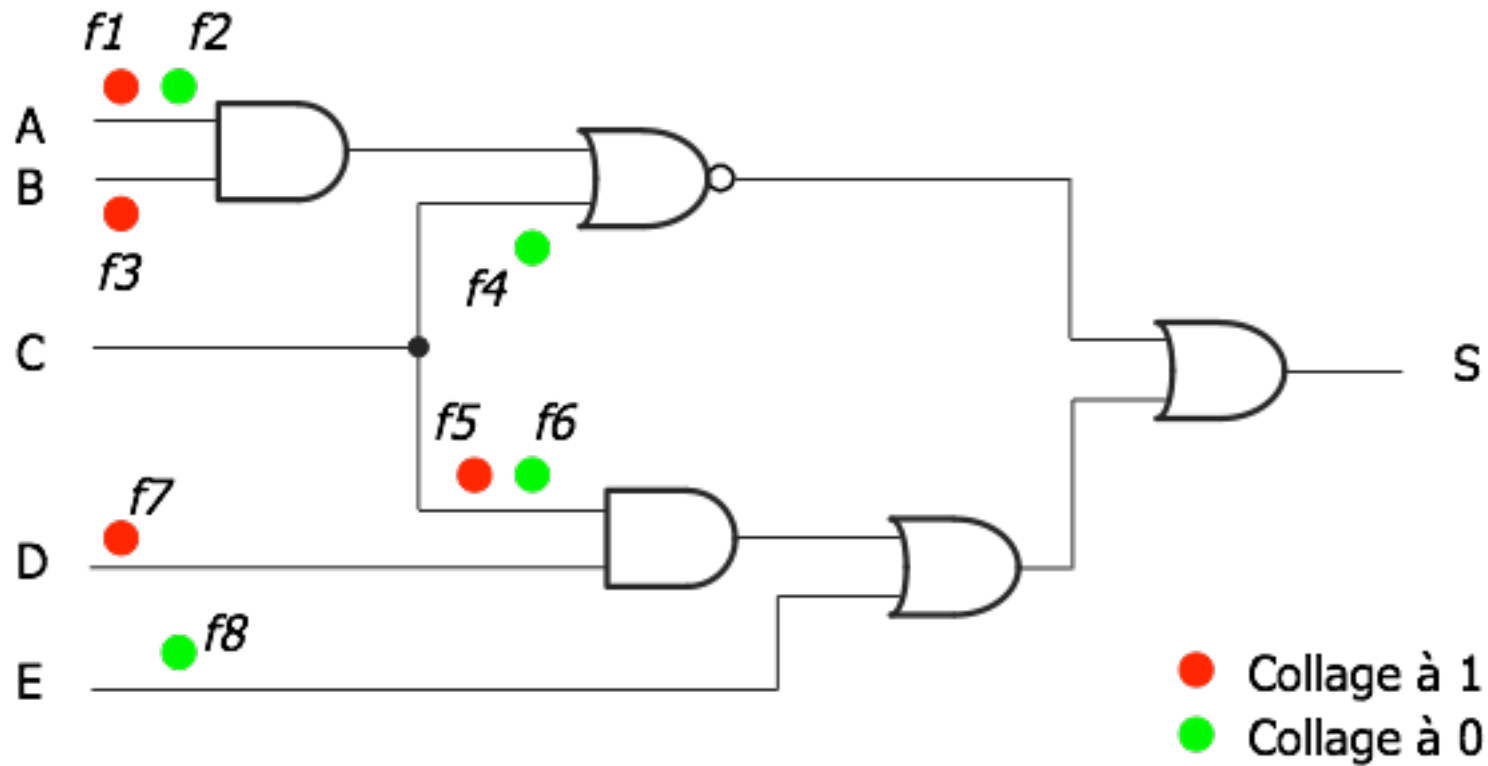
# Exercice


which faults are detected by the input "01110"?





# In practice

- Use of Synopsys© Tetramax

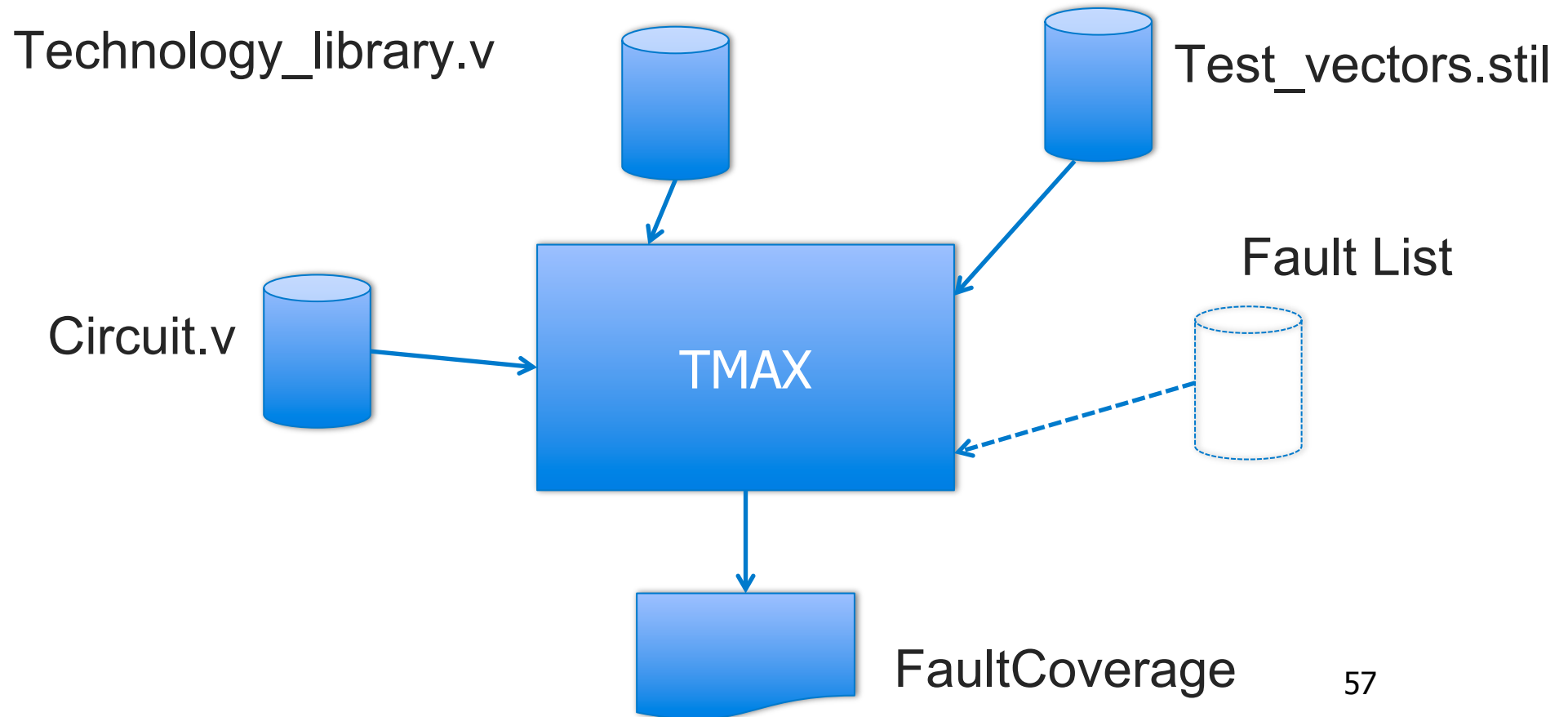

# Invoking TetraMax

- source /soft/Synopsys/source\_config/.config\_tetramax\_standalone\_vI-2013.12
- tmax

```
// is subject to the terms and conditions of a written linc
// between you, or your company, and Synopsys, Inc.
//
//
//*****
Warning: As of the J-2014.09 version of TetraMAX, the 32-bit
the product will not be delivered by default. If you require
version for any reason, please contact Synopsys technical sup

Tcl mode is on by default. Use -notcl to run in native mode.
Executing startup file "/soft/Synopsys/txs_vI-2013.12-SP2/ad
BUILD-T>
```

Log History

BUILD-T> read

Ready Stop Build DRC Test

You can  
enter  
commands



# Step1

---

- Read and Compile the circuit description

```
read_verilog C35.v -library
```

```
read_verilog ex01.v
```

```
run_build_model
```

```
Run_drc
```



## Step 2

---

- Generate the fault list

```
set_faults -model stuck  
add_faults -all
```



## Step 3

---

- Specify the test vectors to be simulated
  - We have to use the stil syntax
  - Look in the example

```
Pattern "_pattern_" {
    W "_default_WFT_";
    "precondition all Signals": C
    { "_pi"=0000; "_po"=XX; }

    "pattern 0": Call "capture" {
        "_pi"=1010; "_po"=LL; }
}
```



## Step 3

---

- Import the test vector file

```
set_patterns -external example_ex01.stil
```

- Now we can run a simulation

```
run_simulation
```

- You will get errors:

```
TEST-T> run_simulation
```

```
Begin good simulation of 1 external  
patterns.
```

```
0 S2 (exp=0, got=1)
```

```
Simulation completed: #patterns=1,  
#fail_pats=1(0), #failing_meas=1(0),  
CPU time=0.00
```



## Step 3

---

- Tmax has to calculate the gold outputs before running the fault simulation

```
run_simulation -override_differences
```

- Now you can run the fault simulation

```
run_fault_sim
```