

Polytech'Montpellier - MEA4 M2 EEA - Systèmes Microélectroniques

Analog IC Design

Building a DC Small-Signal Model of a CMOS Analog Circuit:
a comprehensive guide

Pascal Nouet - 2015/2016 - nouet@lirmm.fr

http://www.lirmm.fr/~nouet/homepage/lecture_ressources.html




Objective / Content

- Demystify the building of a low-frequency (dc) small-signal model for your CMOS analog circuit
- A step by step straightforward approach
- Pre-requisites
 - Good practice of solving electrical circuits (Node and Mesh laws)
 - Large- and small-signal models for MOST in strong-inversion
- Content
 - A comprehensive guide
 - A set of exercises
 - Good practice of solving small-signal circuits





From Norton (Current) Source to MOS transistor


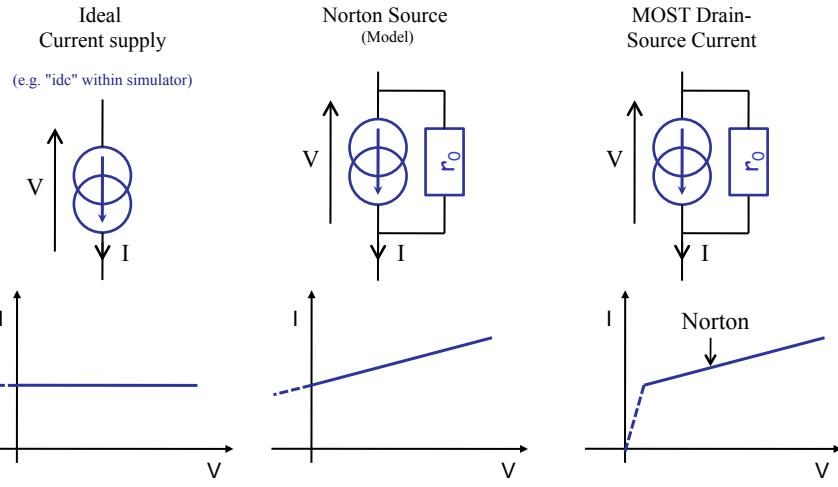
Practical Current Source \neq Current supply



Outline

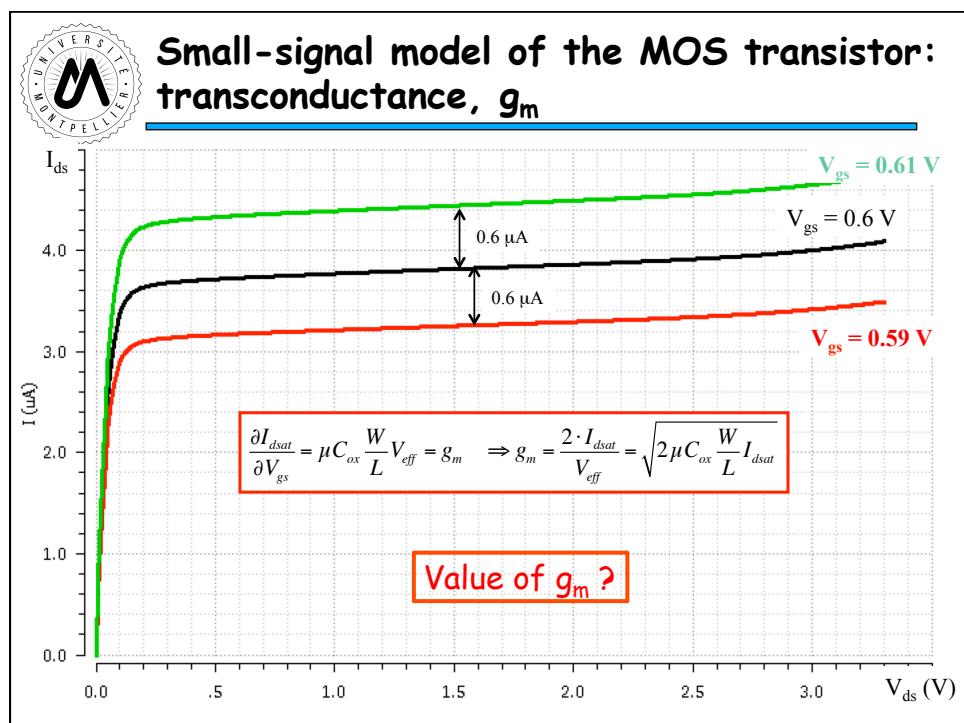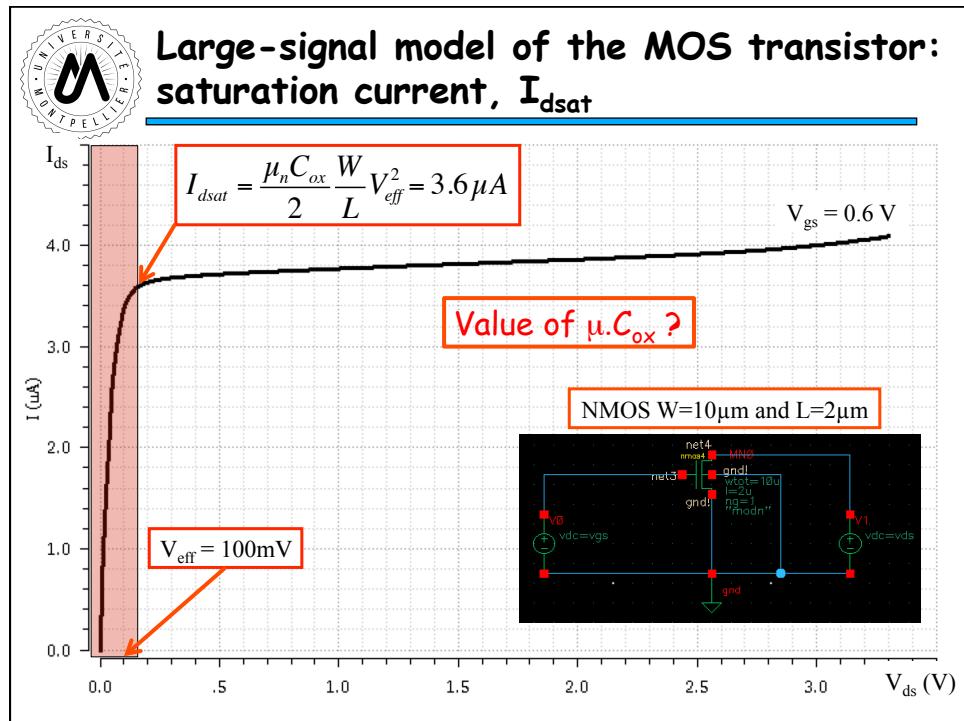- Large- and small-signal models for MOST in strong-inversion
 - Overview of theoretical background
 - Experiments
- DC Small-Signal Model of a CMOS Analog Circuit
 - Step-by-step method
 - Practical example
- Exercises
 - A basic Voltage source : determine V_{dd} dependency
 - A basic Current source : output resistance and V_{dd} dependency
 - A basic amplifier : voltage gain



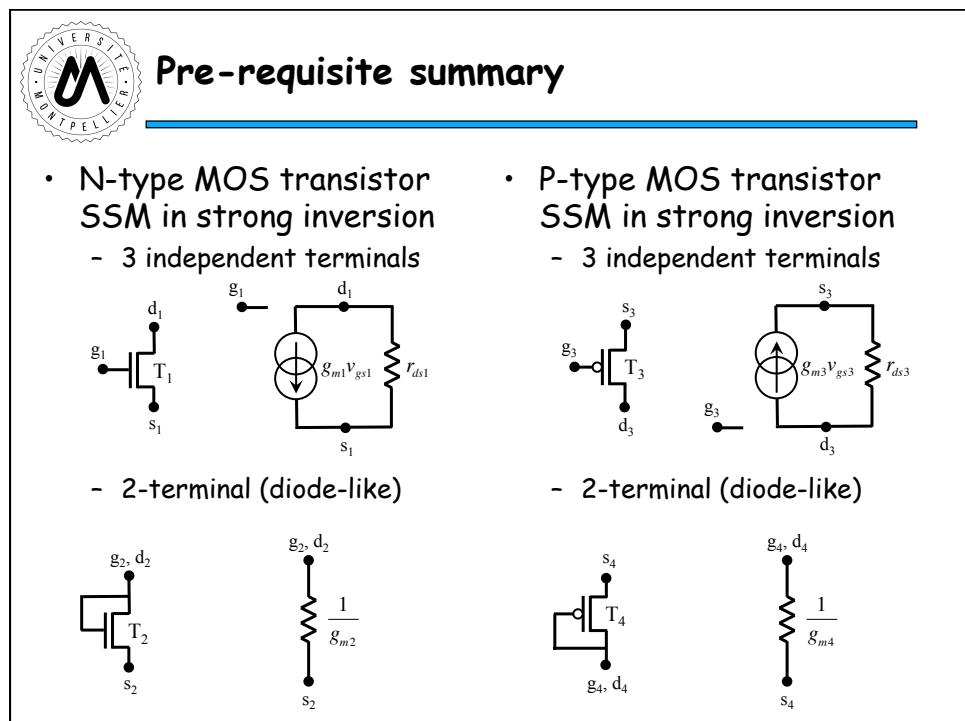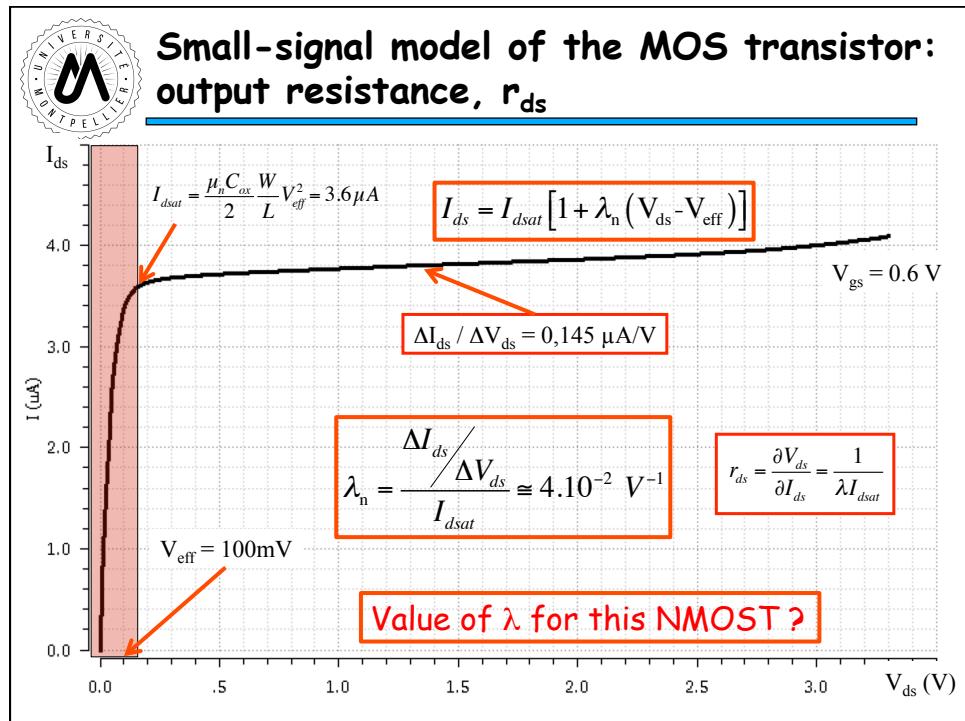




Outline

- Large- and small-signal models for MOST in strong-inversion
 - Overview of theoretical background
 - Experiments
- DC Small-Signal Model of a CMOS Analog Circuit
 - Step-by-step method
 - Practical example
- Exercises
 - A basic Voltage source : determine V_{dd} dependency
 - A basic Current source : output resistance and V_{dd} dependency
 - A basic amplifier : voltage gain



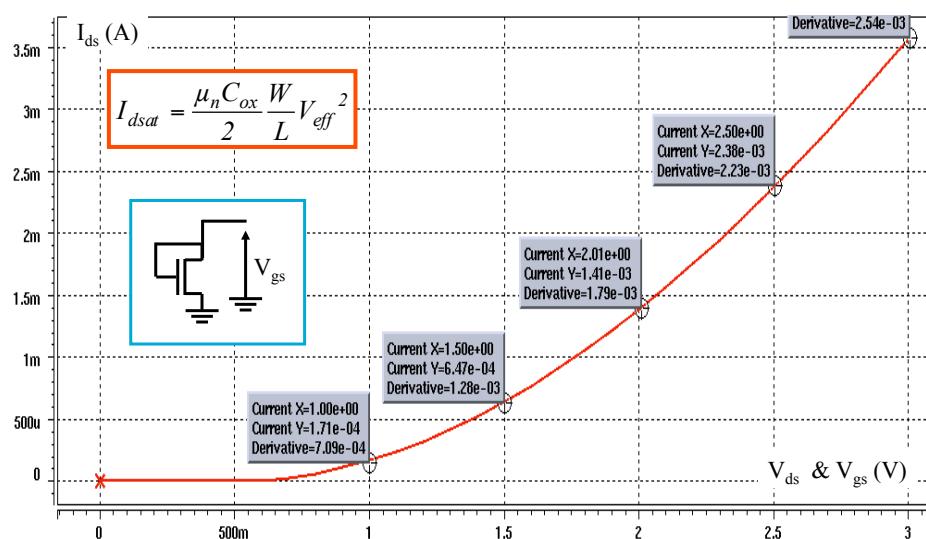Characterization of a diode-connected NMOS Transistor





Characterization of a diode-connected NMOS Transistor

V_{eff} (V)	0.5	1	2
I_{dsat} (μA)	171	647	2380
$\delta I_{ds} / \delta V_{gs}$ (mA/V)	0.709	1.28	2.23
$\mu_n C_{ox}$ (A/V^2)	1.42e-4	1.28e-4	1.12e-4
$\mu_n C_{ox}$ (A/V^2)	1.37e-4	1.29e-4	1.19e-4


$$g_m = \frac{\partial I_{ds}}{\partial V_{gs}} = \mu_n C_{ox} \frac{W}{L} V_{eff} \Rightarrow \mu_n C_{ox} = \frac{g_m}{\frac{W}{L} V_{eff}}$$



$$\mu_n C_{ox} = 2I_{dsat} \left/ \left(\frac{W}{L} V_{eff}^2 \right) \right.$$

$\mu_n \cdot C_{ox} = 112 \text{ to } 142 \mu\text{A/V}^2$



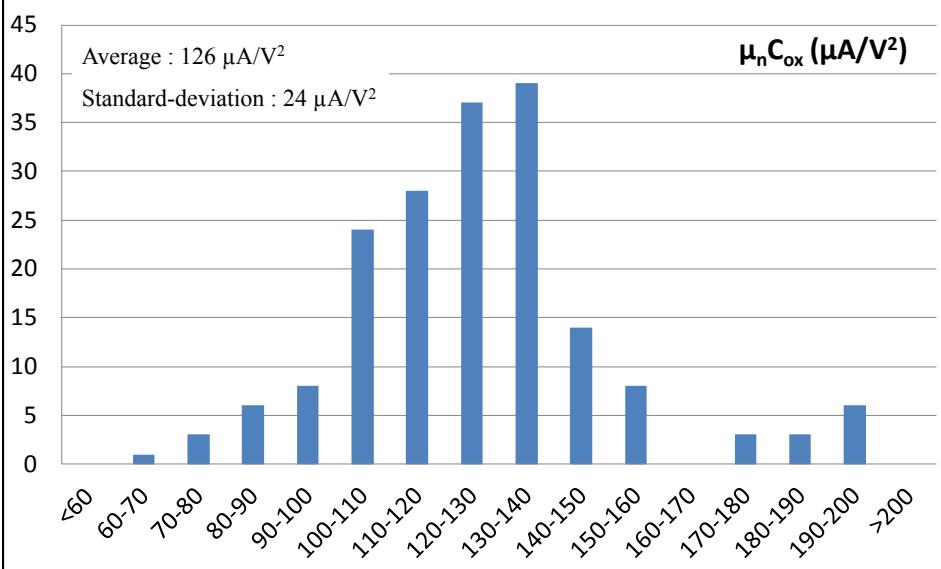Characterization of a diode-connected NMOS Transistor



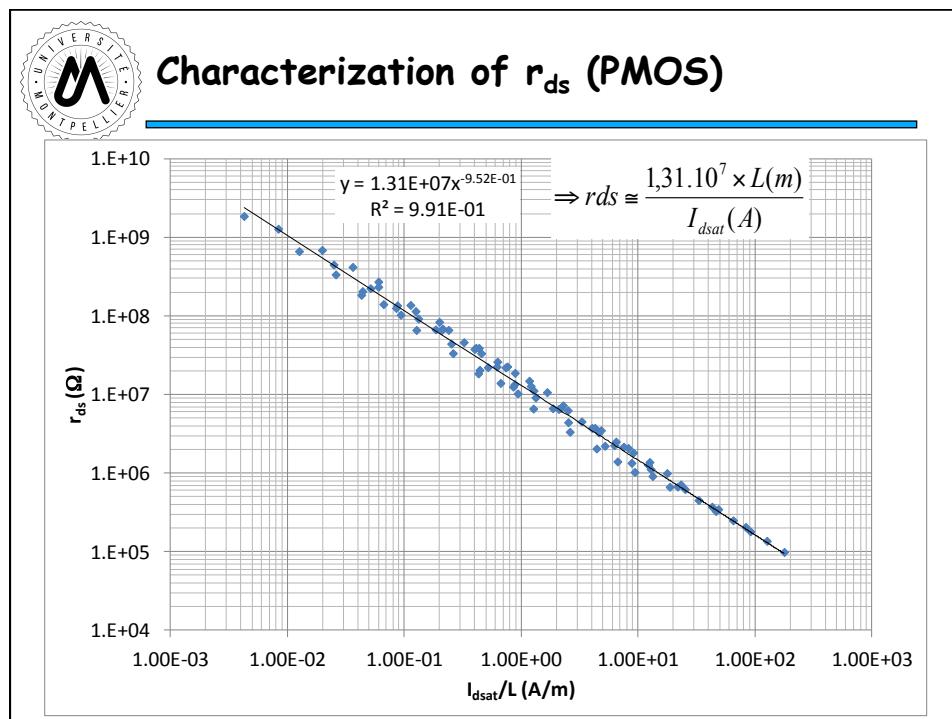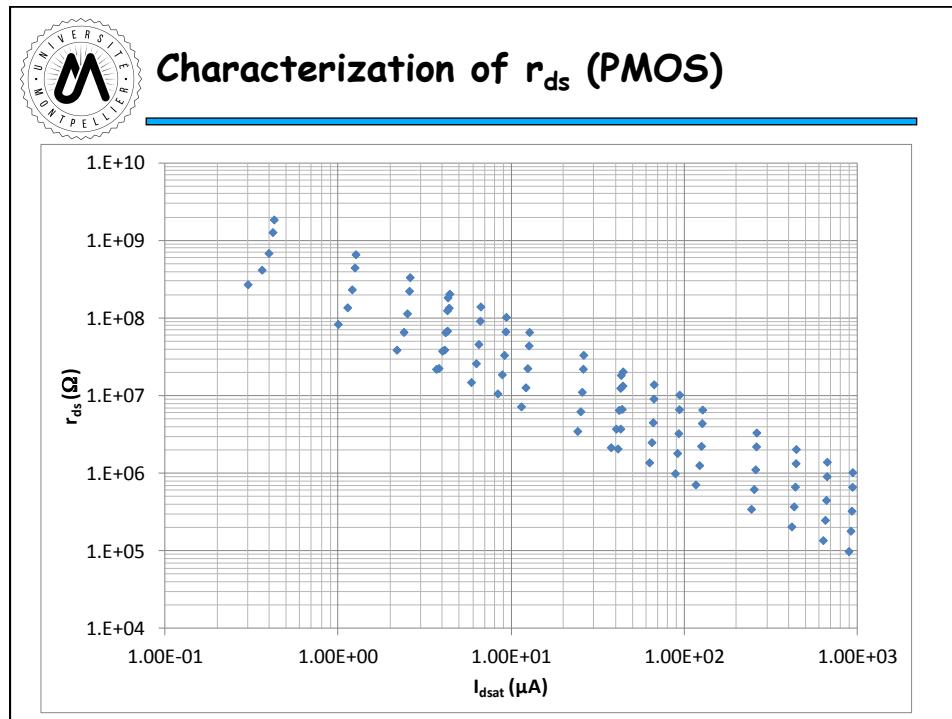



Characterization of λ_p

$$I_{ds} = I_{dsat} \left[1 + \lambda (V_{ds} - V_{eff}) \right] \text{ avec } \lambda = \frac{k_{ds}}{2L_{eff} \sqrt{V_{ds} - V_{eff} + \Phi_0}} \quad k_{ds} = \sqrt{\frac{2\epsilon_0 \epsilon_r}{qN_a}}$$


$$r_{ds} \equiv \frac{13,1 \times L(\mu m)}{I_{dsat}(A)} \Rightarrow \lambda_p = \frac{76mV^{-1}}{L(\mu m)}$$

- Standard deviation

$\pm 25\%$

- Fixed length design
(e.g. $L=10\mu m$)
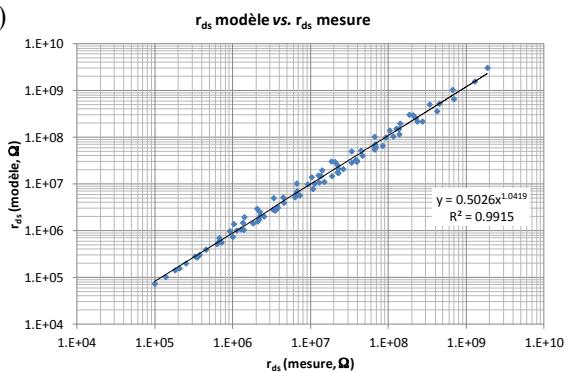
$$\Rightarrow \lambda_p = 7,65 \cdot 10^{-3} V^{-1}$$



Outline


- Large- and small-signal models for MOST in strong-inversion
 - Overview of theoretical background
 - Experiments
- DC Small-Signal Model of a CMOS Analog Circuit
 - Step-by-step method
 - Practical example
- Exercises
 - A basic Voltage source : determine V_{dd} dependency
 - A basic Current source : output resistance and V_{dd} dependency
 - A basic amplifier : voltage gain




Pre-requisite summary

- N-type MOS transistor SSM in strong inversion

- 3 independent terminals

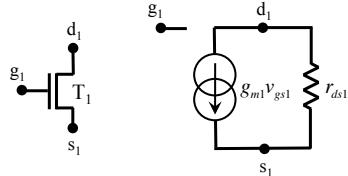


- 2-terminal (diode-like)

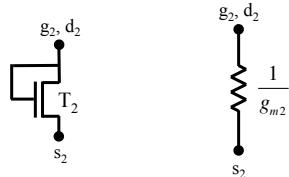


- P-type MOS transistor SSM in strong inversion

- 3 independent terminals

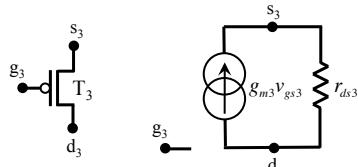

- 2-terminal (diode-like)

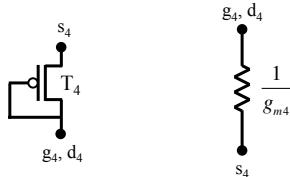

The step-by-step method

- All the steps below will be easier and you will reduce the risk of error if you keep the initial circuit topography for your small-signal model...
- Step 1: identify your input i.e. the magnitude that will vary during your small-signal analysis and keep-it unaltered anytime
- Step 2: replace I and V sources by their small-signal model
- Step 3: replace each transistors by their small-signal model including labels for g, d, s
- Step 4: add electrical connections as in your initial circuit
- Step 5: identify all required v_{gs} and eliminate related voltage-controlled current sources when $v_{gs}=0$
- Step 6: identify your output variable, eventually rearrange your circuit and solve the obtained circuit




Outline

- Large- and small-signal models for MOST in strong-inversion
 - Overview of theoretical background
 - Experiments
- DC Small-Signal Model of a CMOS Analog Circuit
 - Step-by-step method
 - Practical example
- Exercises
 - A basic Voltage source : determine V_{dd} dependency
 - A basic Current source : output resistance and V_{dd} dependency
 - A basic amplifier : voltage gain



Building a small-signal model

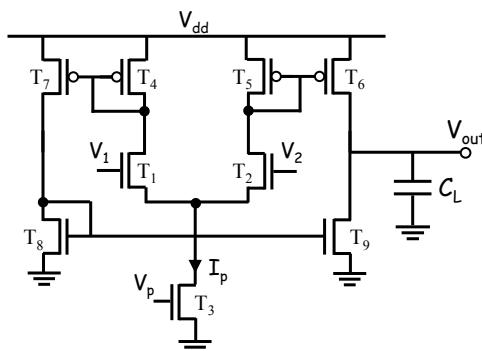- Let's determine the small-signal output resistance of this Operational Transconductance Amplifier






Outline

- Large- and small-signal models for MOST in strong-inversion
 - Overview of theoretical background
 - Experiments
- DC Small-Signal Model of a CMOS Analog Circuit
 - Step-by-step method
 - Practical example
- Exercises
 - A basic Voltage source : determine V_{dd} dependency
 - A basic Current source : output resistance and V_{dd} dependency
 - A basic amplifier : voltage gain



Your first Analog Design

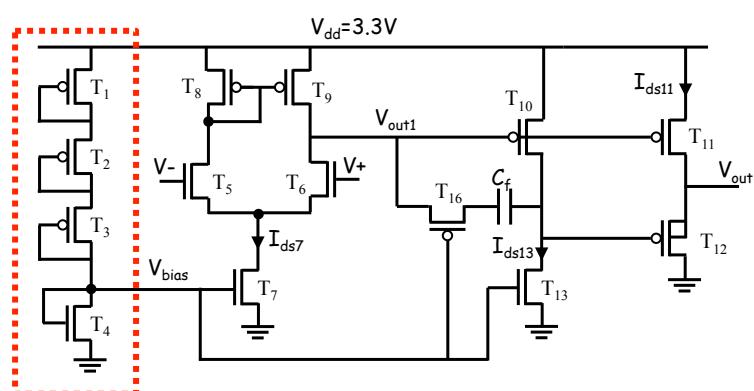

Voltage Reference



Homework & Lab


- Homework
 - Choose size of T_1 to T_4 for $V_{bias}=0.6V$ and $I_{T1}=10\mu A$
 - Derive a small-signal model of the circuit to determine sensitivity to V_{dd} of both V_{bias} and I_{T1}
 - Compute these sensitivities
- Lab
 - Verify the biasing point using an 'Operating Point' simulation (both V_{bias} and I_{T1})
 - Verify the sensitivity to V_{dd} of the biasing point using a 'DC' simulation (both V_{bias} and I_{T1})



Outline

- Large- and small-signal models for MOST in strong-inversion
 - Overview of theoretical background
 - Experiments
- DC Small-Signal Model of a CMOS Analog Circuit
 - Step-by-step method
 - Practical example
- Exercises
 - A basic Voltage source : determine V_{dd} dependency
 - A basic Current source : output resistance and V_{dd} dependency
 - A basic amplifier : voltage gain

 Your first Analog Design

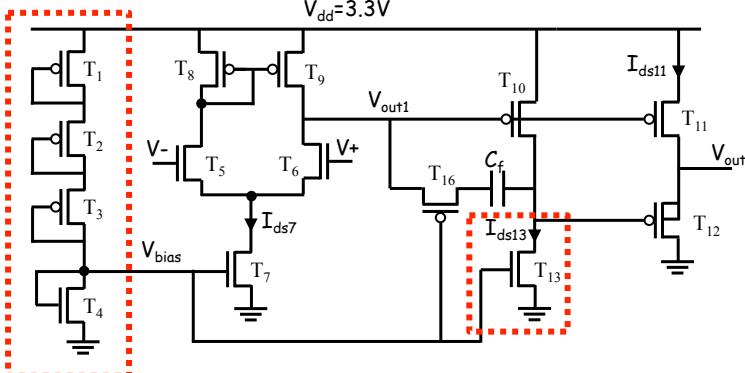

Voltage Reference

Current Source

 Homework & Lab

- Homework
 - Design T_{13} for $I_{T13}=50\mu A$
 - Derive a small-signal model of the circuit to determine r_{out}
 - Compute r_{out}
- Lab
 - Verify the biasing point using an 'Operating Point' simulation (I_{T13})
 - Verify the output resistance using a 'DC' simulation




Outline

- Large- and small-signal models for MOST in strong-inversion
 - Overview of theoretical background
 - Experiments
- DC Small-Signal Model of a CMOS Analog Circuit
 - Step-by-step method
 - Practical example
- Exercises
 - A basic Voltage source : determine V_{dd} dependency
 - A basic Current source : output resistance and V_{dd} dependency
 - A basic amplifier : voltage gain



Your first Analog Design

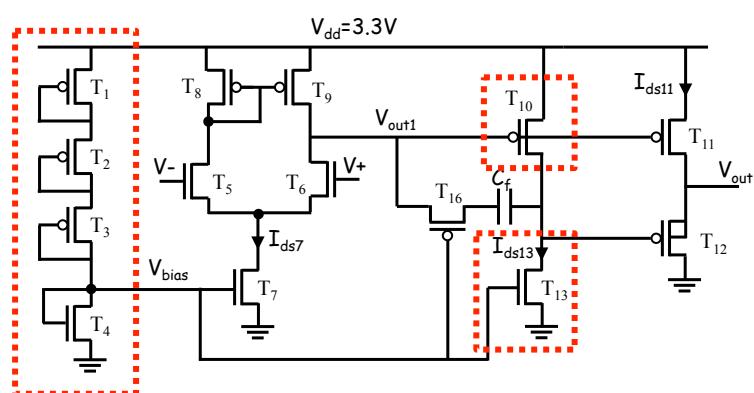

Voltage Reference

Current Source

**Common source
voltage amplifier**



Homework & Lab

- Homework
 - Derive a small-signal model of the circuit to determine the voltage gain
 - Compute the voltage gain
 - Design T_{10} for a voltage gain of 500
- Lab
 - Verify the voltage gain using a 'DC' simulation
 - Verify the voltage gain using a 'AC' simulation



Références

- D. Johns and K. Martin, "Analog Integrated Circuit Design", John Wiley & Sons, Inc. 1997, ISBN 0-471-14448-7
- P. Allen and D. Holberg, "CMOS Analog Circuit Design", 2nd Edition, 2002, Oxford University Press, ISBN 0-19-511644-5
- B. Razavi, "Design of Analog CMOS Integrated Circuits", McGraw Hill, 2001, ISBN 0-07-238032-2
- P. Gray, P. Hurst, S. Lewis, and R.G. Meyer, "Analysis and Design of Analog Integrated Circuits", 4th Edition, John Wiley and Sons, 2001, ISBN 0-471-32168-0