

**Polytech'Montpellier - MEA4  
M2 EEA - Systèmes Microélectroniques**

---

**Analog IC Design**

One- and two-transistors Amplifiers

Pascal Nouet - 2015/2016 - [nouet@lirmm.fr](mailto:nouet@lirmm.fr)




[http://www.lirmm.fr/~nouet/homepage/lecture\\_ressources.html](http://www.lirmm.fr/~nouet/homepage/lecture_ressources.html)


   
## Introduction

---

- Analog Integrated Circuits are based on elementary stages
  - Voltage references
  - Current mirrors
  - Current sources
  - Amplifier stages






## Outline

- Elementary amplifiers
  - Common source amplifier
    - Biasing with a resistor
    - Biasing with an ideal current source
    - Biasing with a current mirror
  - Common gate amplifier
  - Common drain or source follower
  - Overview of Basic CMOS Amplifiers
- Common mode issues
  - Differential pair and differential amplifier
  - Differential output amplifier
- Homework & Labs





 
## Common Source amplifier



- Resistance biasing:  
dimensionnement & plage de fonctionnement
  - $V_{out} > V_{eff}$
  - $V_{in}(dc) \rightarrow V_{eff1} \rightarrow W/L (I_{bias})$
  - $R \rightarrow V_{out} \# V_{dd}/2$
- Small-Signal Model
  - Voltage Gain, input and output resistance



 
$$V_{in} = V_{dc} + v_{in} \cong V_{eff} + V_{in}$$



  

  

 


## Outline

- Elementary amplifiers
  - Common source amplifier
  - Common gate amplifier
  - Common drain or source follower
  - Overview of Basic CMOS Amplifiers
- Common mode issues
  - Differential pair and differential amplifier
  - Differential output amplifier
- Homework & Labs

 **Common gate amplifier**

**All transistors are saturated**

 




$v_{gs1} = -v_{in}$

$$g_{ds2} \cdot v_{out} + g_{ds1} \cdot (v_{out} - v_{in}) - g_{m1} \cdot v_{in} = 0$$

$$(g_{ds1} + g_{ds2}) \cdot v_{out} = (g_{ds1} + g_{m1}) \cdot v_{in} \quad A_v = \frac{v_{out}}{v_{in}} = \frac{g_{m1} + \cancel{X}_1}{g_{ds1} + g_{ds2}}$$


**Input resistance ?**
   
$$r_{in} = \frac{r_{ds2}}{A_v} \cong \frac{2}{g_{m1}}$$




 **Source follower (Common drain)**

**All transistors are saturated**

 



$$V_{gs1} = V_{in} - V_{out}$$

$$V_{out} = \left( r_{ds1} // r_{ds2} \right) \times g_m1 \cdot V_{gs1}$$

$$A_v = \frac{V_{out}}{V_{in}} = \frac{g_m1}{g_{ds1} + g_{ds2} + g_m1} \approx 1$$

$$r_{out} = \frac{1}{g_{ds1} + g_{ds2} + g_m1} \approx \frac{1}{g_m1}$$

**Output resistance?**





 
 


## Outline

- Elementary amplifiers
  - Common source amplifier
  - Common gate amplifier
  - Common drain or source follower
  - Overview of Basic CMOS Amplifiers
- Common mode issues
  - Differential pair and differential amplifier
  - Differential output amplifier
- Homework & Labs



## Overview of Basic CMOS Amplifiers

      




## Outline

- Elementary amplifiers
  - Common source amplifier
  - Common gate amplifier
  - Common drain or source follower
  - Overview of Basic CMOS Amplifiers
- Common mode issues
  - Differential pair and differential amplifier
  - Differential output amplifier
- Homework & Labs



## Common Source Amplifier Limitations

### Current Mirror Biasing

 


$$A_V = -g_{m1} \left( r_{ds1} // r_{ds2} \right) = \frac{-g_{m1}}{(g_{ds1} + g_{ds2})}$$

$$r_{in} = \infty$$

$$r_{out} = r_{ds1} // r_{ds2}$$


### • Biasing

$$- V_{in} = V_{eff} + V_{th}$$

 



## Differential Input Stage: Principle

 


- Sizing: symmetrical**
- Biassing**
  - $I_{dsat} = I_{bias}/2$
  - $V_{in+} = V_{in-} = V_{mc}$
  - $V_{s1} = V_{s2} > V_{min}(I_{bias})$
  - $V_{gs1} = V_{gs2} = V_{eff} + V_{tn}$
  - $V_{out} = V_{dd} - R_{load} \cdot I_{bias}/2$
- Small-signal**
  - $v_{ind} = V_{in+} - V_{in-}$
  - $v_{out} = V_{out+} - V_{out-}$
  - $v_{mc} = (v_{in+} + v_{in-})/2$

$$A_{vd} = \frac{v_{out}}{v_{ind}} = \frac{V_{out+} - V_{out-}}{v_{ind}} = g_m R_{load}$$

$$A_{ymc} = \frac{v_{out}}{v_{mc}} = \frac{V_{out+} - V_{out-}}{v_{mc}} = 0$$



## Differential Input Stage: Principle

 

**Differential mode**

$$I_{d1} = I_{d2} = \frac{I_{bias}}{2}$$

$$V_{in+}^+ = V_{mc} + \frac{V_{in}}{2}$$

$$V_{in-}^- = V_{mc} - \frac{V_{in}}{2}$$


$$V_{eff1} = V_{eff2}$$

$$g_{m1} = g_{m2} = g_m$$

$$v_{in+}^+ = -v_{in-}^- = \frac{v_{ind}}{2}$$


$$v_{gs1} = -v_{gs2}$$

$$g_m v_{gs1} = -g_m v_{gs2}$$
 
$$i_s = 0$$



 
## Differential Input Stage: high gain implementation





- Active load with a current mirror
  - Higher output resistance
  - Referenced output voltage
- Biasing
  - $V_{out} = V_{dd} - V_{gs3}$

$$A_{vd} = \frac{V_{out}}{V_{ind}} = g_m r_{out}$$

$$A_{vmc} = \frac{V_{out}}{V_{mc}} = 0$$


  
## Differential Input Stage: small-signal output resistance



$$v_{in} = 0$$


$$v_{gs4} = 0$$

$$g_{m4} v_{gs4} = 0$$

$$r_{out} = r_{ds2} // r_{ds4}$$


 
## Differential Input Stage: small-signal output voltage



$$v_{out} = \left( g_{m4} v_{gs4} + g_m \frac{v_{in}}{2} \right) \times (r_{ds2} // r_{ds4})$$

$$v_{gs4} \approx g_m \frac{v_{in}}{2} \times \frac{1}{g_{m3}}$$

$$v_{out} = \left( \frac{g_{m4}}{g_{m3}} g_m \frac{v_{in}}{2} + g_m \frac{v_{in}}{2} \right) \times (r_{ds2} // r_{ds4})$$

$$g_{m3} = g_{m4}$$

$$V_{in}^+ = V_{mc} + \frac{v_{in}}{2}$$

$$V_{in}^- = V_{mc} - \frac{v_{in}}{2}$$

$$\frac{v_{out}}{v_{in}} = g_m \times (r_{ds2} // r_{ds4})$$



## Differential Input Stage: small-signal gain analysis

$$\frac{v_{out}}{v_{in}} = g_{m1,2} \times (r_{ds2} // r_{ds4}) = \frac{g_{m1,2}}{g_{ds2} + g_{ds4}}$$


$$A_v = \frac{g_{m1,2}}{\lambda_n \frac{I_{bias}}{2} + \lambda_p \frac{I_{bias}}{2}}$$

$$g_{m1,2} = \frac{2 \left( \frac{I_{bias}}{2} \right)}{V_{eff1,2}} = \frac{I_{bias}}{V_{eff1,2}}$$

$$A_v = \frac{2}{(\lambda_n + \lambda_p) V_{eff1,2}}$$

$$V_{eff1,2} = \sqrt{\frac{2 I_{d1,2} L}{\mu_n C_{ox} W}} \quad A_v = \frac{\sqrt{2 \mu_n C_{ox}}}{(\lambda_n + \lambda_p) \cdot \sqrt{I_{d1,2}}} \sqrt{\frac{W}{L}}_{1,2}$$

 Low  $V_{eff}$  and large length for large gain





## Differential Input Stage: common-mode input range (CMIR)



All transistors must operate in saturation:

Low  $V_{eff}$  for large CMIR

$$V_B = V_{dd} - |V_{eff3,4}| - |V_{tp}|$$

$$V_B - V_A > V_{eff1,2}$$

$$V_A > V_{A,min}$$

$$V_A = V_{mc} - (V_{in} + V_{eff1,2}) > V_{A,min}$$

$$\Rightarrow V_{mc} > V_{A,min} + V_{in} + V_{eff1,2}$$


$$V_B - V_A > V_{eff1,2} \rightarrow V_B > V_{eff1,2} + V_A$$

$$V_B > (V_{mc} - V_A - V_{in}) + V_A$$

$$V_B > V_{mc} - V_{in}$$

$$V_{mc} < V_B + V_{in}$$

$$\Rightarrow V_{mc} < V_{dd} - |V_{eff3,4}| - |V_{tp}| + V_{in}$$

 


## Outline

- Elementary amplifiers
  - Common source amplifier
  - Common gate amplifier
  - Common drain or source follower
  - Overview of Basic CMOS Amplifiers
- Common mode issues
  - Differential pair and differential amplifier
  - Differential output amplifier
- Homework & Labs



## Homework & Lab

 


### Dimensionnement de l'étage différentiel

- 1°) Calculez le W/L de  $T_{13}$  et  $T_{14}$  de façon à ce que la tension de sortie soit égale à 2,5V lorsque  $V_1=V_2=1,6V$ . Estimez ensuite la résistance de sortie de cet étage.
- 2°) Calculez le W/L de  $T_{11}$  et  $T_{12}$  de façon à ce que le gain différentiel soit de 500.
- 3°) Quelle serait la fréquence de coupure de cet étage si on connecte une capacité de 5 pF à la sortie à la place du 2<sup>ème</sup> étage de gain ?



## Homework & Lab

 

### Dimensionnement du 2<sup>ème</sup> étage de gain

- 1°) Calculez la résistance de sortie de l'étage puis le W/L du transistor  $T_{15}$  ainsi que le gain petit-signal de l'étage  $A_v$ .
- 2°) On connecte une résistance de 100kΩ en sortie de l'amplificateur. Calculez le nouveau gain de l'étage  $A'_v$  ?



## Homework & Lab

### Performances statiques de l'OTA Miller

Déterminez les valeurs théoriques du gain statique (petit-signal) de l'amplificateur (en l'absence de charge), de la plage de mode commun d'entrée admissible et de la dynamique de sortie.

### Caractérisation statique de l'OTA Miller

Tracez la caractéristique statique  $V_S = f(V_+ - V_-)$  sans charge de sortie pour un mode commun égal à  $V_{dd}/2$ . Relevez le point de pente maximum  $(V_+ - V_-)_{max}$  de cette caractéristique et déduisez-en le gain expérimental.

### Caractérisation dynamique de l'OTA Miller

Tracez le diagramme de Bode du montage et concluez sur la stabilité de ce montage utilisé en suiveur de tension.

Montez l'amplificateur en suiveur de tension puis appliquez un échelon de tension entre 1V et 2V sur l'entrée et observez la sortie. Conclure et expliquez les résultats obtenus.