

**Polytech'Montpellier - MEA4  
M2 EEA - Systèmes Microélectroniques**

**Analog IC Design**

**Miller Operational Transconductance Amplifier &  
Miller Operational Amplifier**

Pascal Nouet - 2015/2016 - nouet@lirmm.fr

[http://www.lirmm.fr/~nouet/homepage/lecture\\_ressources.html](http://www.lirmm.fr/~nouet/homepage/lecture_ressources.html)






**Introduction**

$$V_+ = V_{mc} + \frac{v_{in}}{2}$$

$$V_- = V_{mc} - \frac{v_{in}}{2}$$

$$v_{in} = V_+ - V_-$$

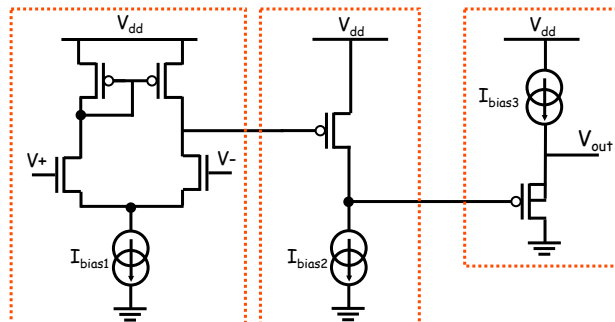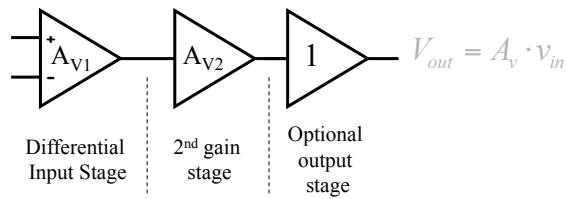




## Outline


---

- Introduction
- AOP assembly
- Dynamic behavior
- AOP stability
- AOP compensation
- Homework & Labs



## AOP assembly

---

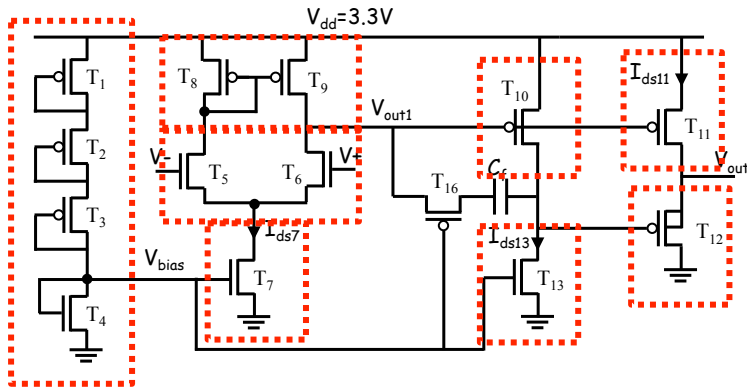

**Voltage reference**


**Current sources**

**Differential pair**

**Active load**

**Common source**

**Common drain**



## AOP assembly: connecting first stage to the second

---


$I_{ds13} = I_{d7}$

$V_{eff7} = V_{eff13}$

$I_{ds10} = 2I_{d8,9}$

$V_{eff10} = V_{eff8,9}$


$\left. \frac{W}{L} \right|_{10} = 2 \left. \frac{W}{L} \right|_{8,9}$

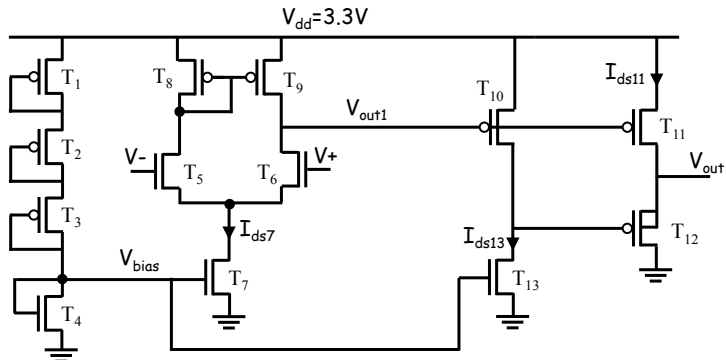

$A_{v1} = \frac{v_{out1}}{v_{ind}} = - \frac{g_{m6}}{g_{ds6} + g_{ds9}}$

$A_{v2} = \frac{v_{out}}{v_{out1}} = - \frac{g_{m10}}{g_{ds10} + g_{ds13}}$

$\Rightarrow$   **$g_{m10}$**  (and so 2<sup>nd</sup> stage gain) depends on the first stage design ( $V_{eff8,9}$ )



## Total dc gain

---

$A_{v1} = \frac{v_{out1}}{v_{ind}} = - \frac{g_{m6}}{g_{ds6} + g_{ds9}}$

$g_{ds6} = \lambda_n \frac{I_{ds7}}{2}$

$g_{ds9} = \lambda_p \frac{I_{ds7}}{2}$

$g_{m6} = \frac{2 \frac{I_{ds7}}{2}}{V_{eff6}} = \frac{I_{ds7}}{V_{eff6}}$

$A_{v2} = \frac{v_{out}}{v_{out1}} = - \frac{g_{m10}}{g_{ds10} + g_{ds13}}$


$g_{ds10} = \lambda_p I_{ds13}$

$g_{ds13} = \lambda_n I_{ds13}$

$g_{m10} = \frac{2I_{ds13}}{V_{eff10}}$


$A_v = A_{v1} \times A_{v2}$

$$A_v = \frac{4}{(\lambda_n + \lambda_p)^2 V_{eff6} V_{eff10}}$$




## AOP assembly: connecting 2<sup>nd</sup> stage to the output stage

---

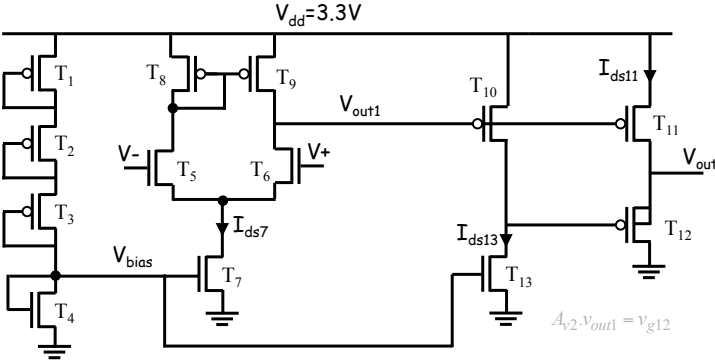


- $V_{gs11}$  is fixed by connecting  $T_{11}$  gate to the reference voltage stage or to  $V_{out1}$  which variations are much smaller than those of  $V_{g12}$



## Outline

---

- Introduction
- AOP assembly
- Dynamic behavior
- AOP stability
- AOP compensation
- Homework & Labs





## Dynamic behavior

---

- Miller OTA is a two-stage amplifier with high output impedance
  - DC gain
 

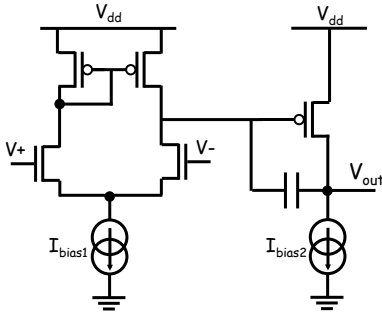
$$A_{v1} \cong -\frac{g_{m1}}{g_{out1}} \quad A_{v2} \cong -\frac{g_{m2}}{g_{out2}}$$
- Open-Loop Dynamic Performances
  - Slew-Rate (V/s) : **SR**
  - Unity-gain frequency (MHz) :  **$f_u$**
  - Cut-off frequency / bandwidth (kHz) :  **$f_c$**
  - Gain-Bandwidth product (MHz) : **GBW**  
for a first order behaviour,  $GBW=f_u$





## MOSFET intrinsic capacitances

---

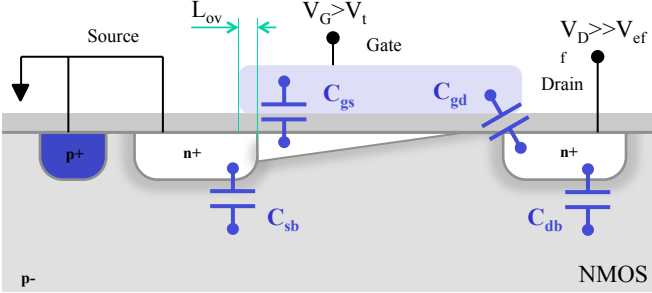

**Gate Capacitances**


$$C_{gs} \approx \left(\frac{2}{3}WLC_{ox}\right) + (WL_{ov}C_{ox})$$

$$C_{gd} \approx (WL_{ov}C_{ox}) \quad L_{ov} \approx \frac{L}{10}$$

**Junction Capacitance (reverse bias)**

$$C_{sb} \approx (A_s + A_{ch})C_{js} \quad C_{jx} \approx \frac{C_{j0}}{\sqrt{1 + \frac{V_{xb}}{\psi_0}}}$$


$$C_{db} \approx A_d C_{jd}$$




## MOSFET dynamic small-signal model

---

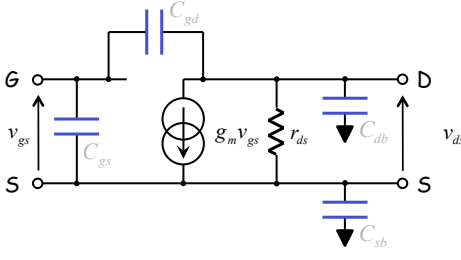
**MOS Transistor "Small Signal" model for dynamic analysis**





## First Pole Analysis

---

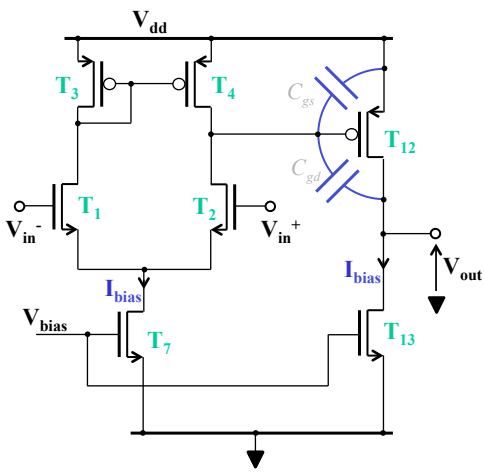

$$A_{v1} = \frac{v_A}{v_{in}} = - \frac{g_{m1}}{g_{ds2} + g_{ds4} + g_{in12}}$$


$g_{in12} = ?$

$C_{d4}, C_{d2}$

$C_{gd12} = 10\% \cdot C_{g12}$


$C_{gs12} = \frac{2}{3} \cdot C_{g12}$

$C_{g12} = C_{oxp} \cdot W_{12} \cdot L_{12}$



## Miller Transformation

---

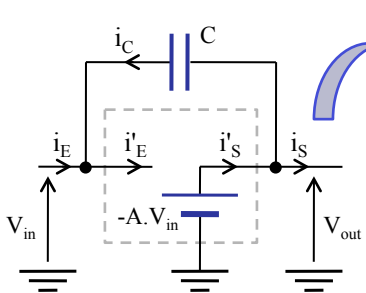


**Input Current**

$$i_E = -i_C + i'_E \quad i_C = Cp(V_{out} - V_{in})$$

$$i_E = -CpV_{out} + CpV_{in} + i'_E$$


$$i_E = CpV_{in}(1 + A) + i'_E$$

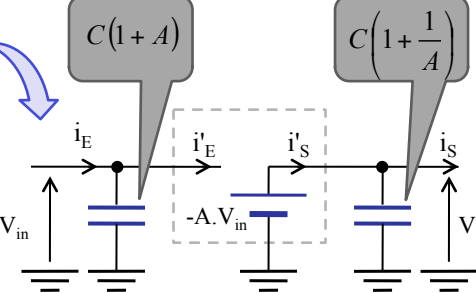

**Output Current**

$$i'_S = i_C + i_S = Cp(V_{out} - V_{in}) + i_S$$

$$i'_S = CpV_{out}\left(1 + \frac{1}{A}\right) + i_S$$




## Miller Transformation


---

With  $A > 0$  et  $|A| \gg 1$ :


$$C(1 + A) \approx C \times |A|$$
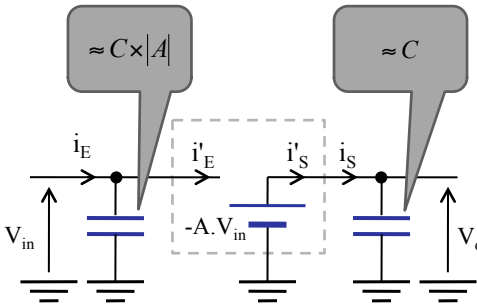
$$C\left(1 + \frac{1}{A}\right) \approx C$$





## Pole due to First Stage Output

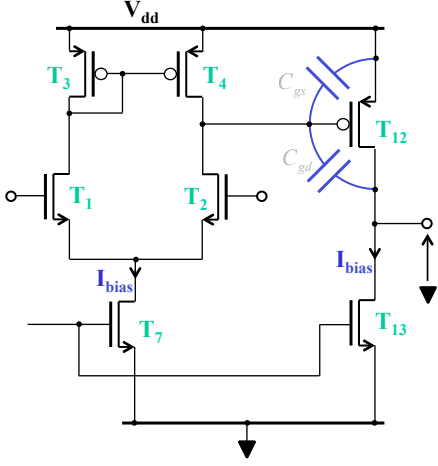


$$A_{v1} = \frac{v_A}{v_{in}} = - \frac{g_{m1}}{g_{ds2} + g_{ds4} + g_{in12}}$$

$$g_{in12} = C_{gs}p + |A_{v2}|C_{gd}p$$

$$g_{in12} = \underbrace{(C_{gs} + |A_{v2}|C_{gd})p}_{C_{in12}}$$
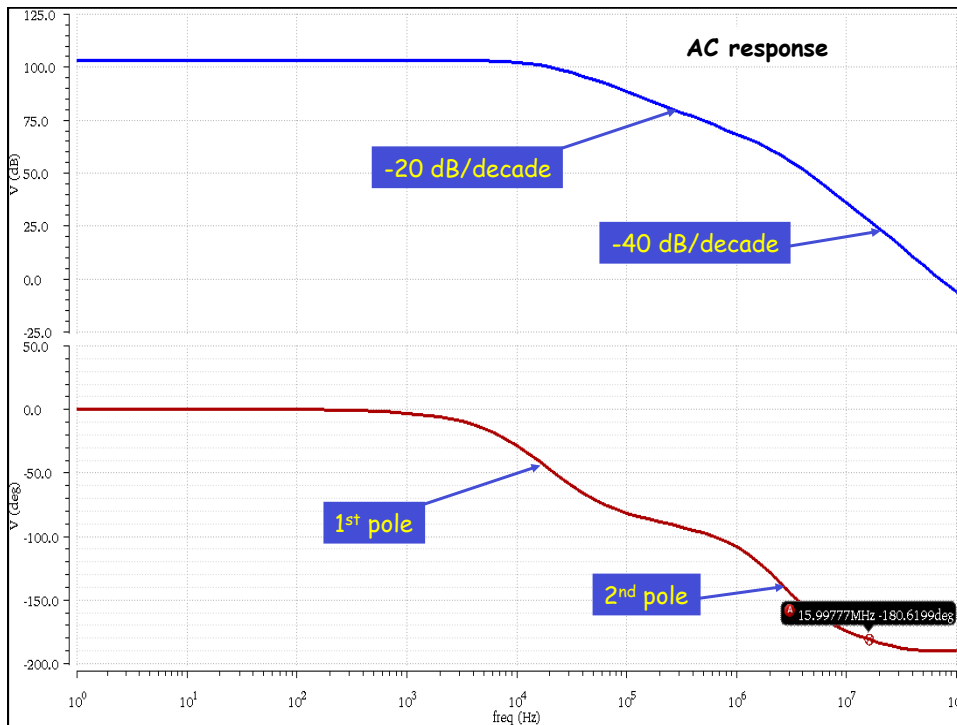
$$A_{v1} = - \frac{g_{m1}}{g_{ds2} + g_{ds4}} \times \frac{1}{\left(1 + \frac{C_{in12}}{(g_{ds2} + g_{ds4})}p\right)}$$







## Outline


---



- Introduction
- AOP assembly
- Dynamic behavior
- AOP stability
- AOP compensation
- Homework & Labs



## Voltage follower

---

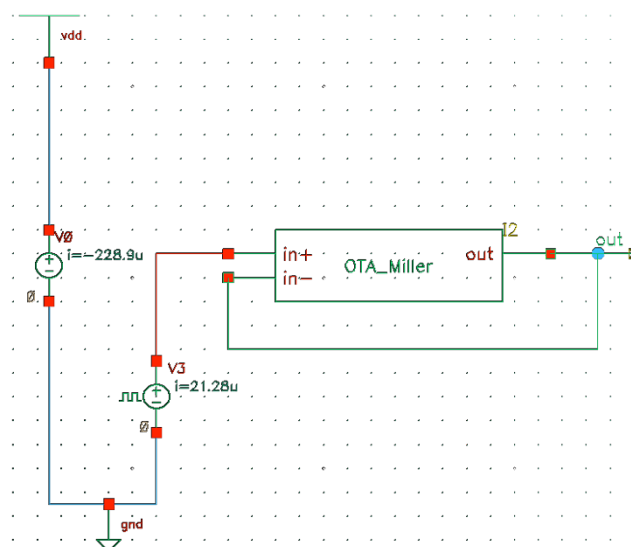

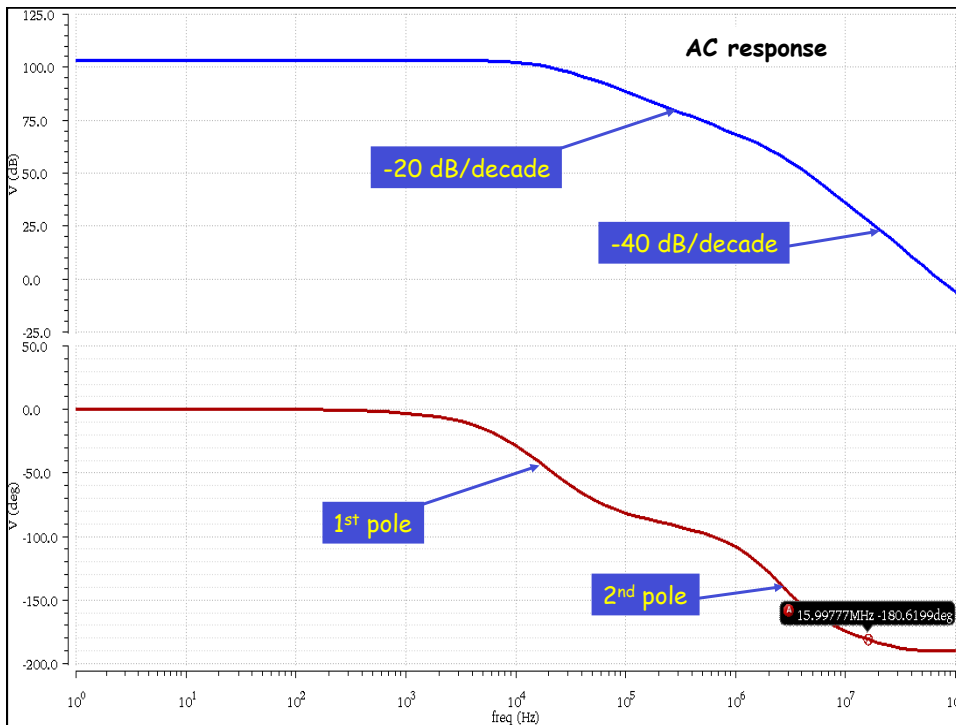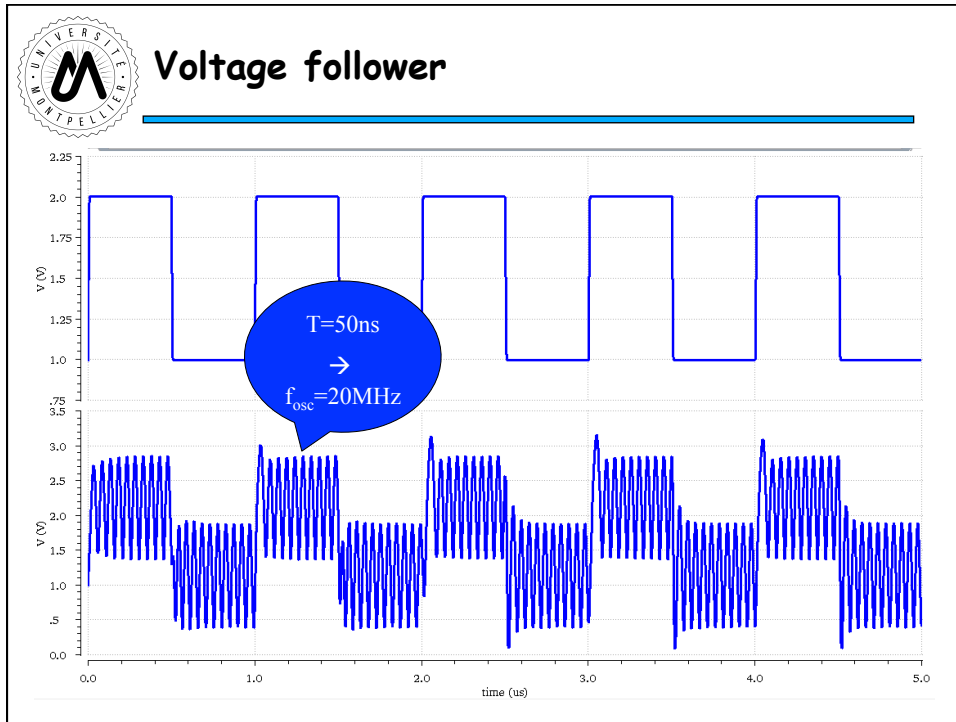



## Summary

---


- Simplified Model
  - One stage  $\rightarrow$  One pole
  - First stage pole is dominant (Miller Effect)
  - A two stage Amplifier should be stable...
- Simulation
  - AC simulations :  $f_c$ ,  $f_u$  and  $GBW$
  - Other poles (current source, ...)
  - Often, a two stage amplifier is not naturally stable



## Outline

---

- Introduction
- AOP assembly
- Dynamic behavior
- AOP stability
- AOP compensation
- Homework & Labs



## Dominant pole adjustment

- Idea: 1<sup>st</sup> pole shifts down to low frequencies by adding  $C_f$  in parallel with  $C_{gd12}$



$$C_f \gg C_{gd12} \Rightarrow C_{total} \approx |A_{v2}| \cdot C_f \Rightarrow \tau \approx \frac{C_{total}}{g_{ds2} + g_{ds4}}$$


$$\Rightarrow f_{c1} = \frac{1}{2\pi\tau} = \frac{g_{ds2} + g_{ds4}}{|A_{v2}| \cdot 2\pi \cdot C_f}$$

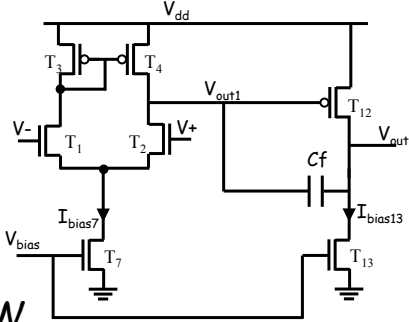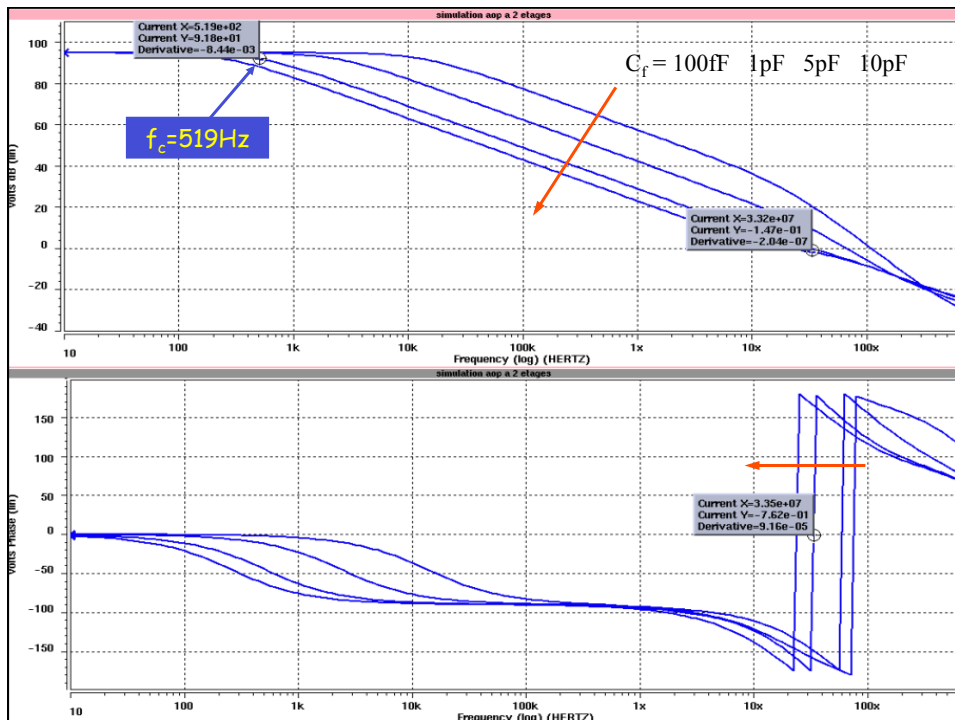example:  $f_{c1} = 500\text{Hz}$

$$\Rightarrow C_f = \frac{3,6 \cdot 10^{-6}}{227,2\pi \cdot 500} = 5\text{pF}$$


- Amplifier behaves like a first order circuit  $\rightarrow$  GBW



### Close-up view of the Miller effect

---

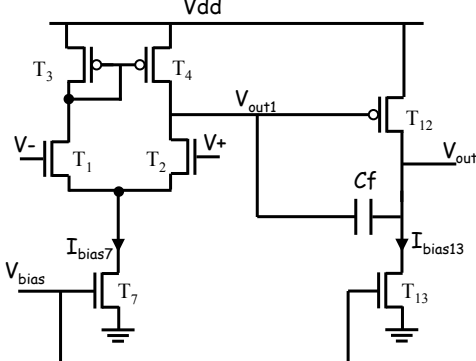


$$r_1 \Rightarrow g_{ds2} // g_{ds4}$$

$$C_1 \Rightarrow C_{d2} + C_{d4} + C_{gs12}$$

$$r_2 \Rightarrow g_{ds12} // g_{ds13} // g_{load}$$


$$C_2 \Rightarrow C_{d12} + C_{d13} + C_{load}$$

$$C_c \Rightarrow C_f + C_{gd12}$$





### Close-up view of the Miller effect

---

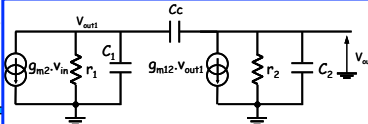

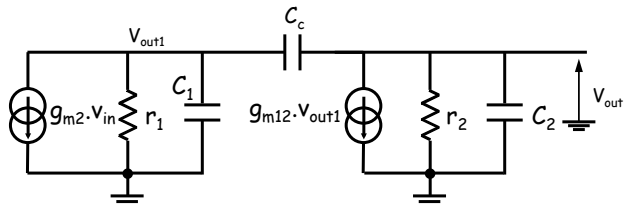
$$-g_{m2} \cdot v_{in} = \frac{v_{out1}}{r_1} + C_1 p \cdot v_{out1} + C_c p \cdot (v_{out1} - v_{out}) \Rightarrow v_{out1} = f(v_{in}, v_{out})$$





## Close-up view of the Miller effect

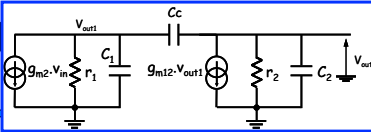

$$\frac{v_{out}}{v_{in}} = \frac{g_{m2}r_1 \cdot g_{m12}r_2 \cdot \left(1 - \frac{C_c P}{g_{m12}}\right)}{1 + ap + bp^2}$$

$$1 + ap + bp^2 = \left(1 + \frac{P}{\omega_{p1}}\right) \left(1 + \frac{P}{\omega_{p2}}\right)$$


}

$$f_{p1} = \frac{1}{2\pi \cdot r_1 g_{m12} r_2 C_c}$$

$$f_{p2} = \frac{g_{m12}}{2\pi \cdot (C_1 + C_2)}$$

$$f_z = \frac{-g_{m12}}{2\pi \cdot C_c}$$

- Increasing  $C_c$ 
  - $f_z$  and  $f_{p1}$  are shifted down accordingly
- Increase of  $g_{m12}$ 
  - silicon cost, power consumption
- Design Tip : higher  $g_{m12}$  increases stability




## Close-up view of the Miller effect

- Solution: adding a serial resistance
  - 1<sup>st</sup> and 2<sup>nd</sup> poles doesn't move a lot
  - Additional 3<sup>rd</sup> pole @ higher frequencies
  - Zero is changed:

$$f_z = \frac{-1}{2\pi \cdot C_c (1/g_{m12} - R_s)}$$

→ Zero can be adjusted

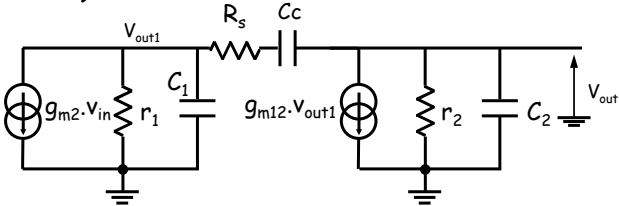
- to compensate 2<sup>nd</sup> pole (not robust enough)
- just after the unity gain frequency (viable solution)




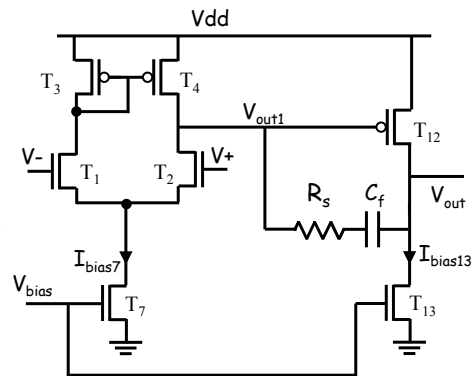
## Zero positioning for stability: first method

- Step 1:
  - First simulation with random  $C_{f0}$  (5pF) and  $R_s=0$
  - Choice of a phase margin
    - extract  $f_u$
    - measure  $A_v(f_u)$
- Step 2:
  - Calculation of  $C_f = C_{f0} \cdot A_v(f_u)$
  - Zero positioning @  $f_u + 20\%$ 
    - $R_s$  calculation



## Zero positioning for stability: 2nd method

- 2nd method:
  - Choice of unity-gain frequency:
    - Example: from initial  $f_u=18\text{MHz}$  →  $f_u = 10\text{MHz}$
  - Calculation of the capacitance:
 
$$C_f = \frac{g_{m2}}{2\pi f_u}$$
  - Zero positioning
    - $f_u + 20\%$  : 12MHz →

$$f_z = \frac{-1}{2\pi \cdot C_c (1/g_{m12} - R_s)} = 12\text{MHz} \Rightarrow R_s = \frac{1}{2\pi f_z \cdot C_c} + \frac{1}{g_{m12}}$$




## Outline

- Introduction
- AOP assembly
- Dynamic behavior
- AOP stability
- AOP compensation
- Homework & Labs



## Homework & Lab

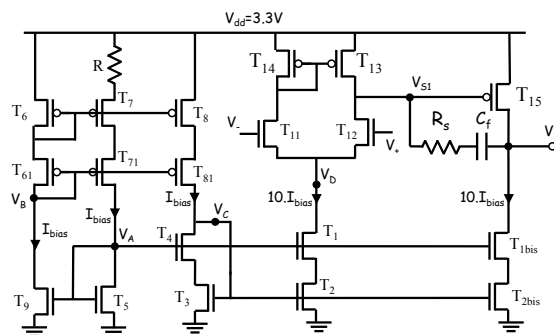

### Caractérisation dynamique de l'OTA Miller

Tracez le diagramme de Bode du montage et concluez sur la stabilité de ce montage utilisé en suiveur de tension. Proposez un circuit de compensation pour cet amplificateur puis tracez à nouveau le diagramme de Bode du montage. En déduire les marges de gain et de phase de cet amplificateur utilisé en montage suiveur.

Montez l'amplificateur en suiveur de tension puis appliquez un échelon de tension entre 1V et 2V sur l'entrée et observez la sortie. Conclure et expliquez les résultats obtenus.