



Chapter 3

Fault Simulation

Arnaud Virazel


virazel@lirmm.fr



Objectives

- To determine the circuit behaviour in presence of each of the faults
- To determine the set of faults detected by a test vector sequence

Fault Simulation flow

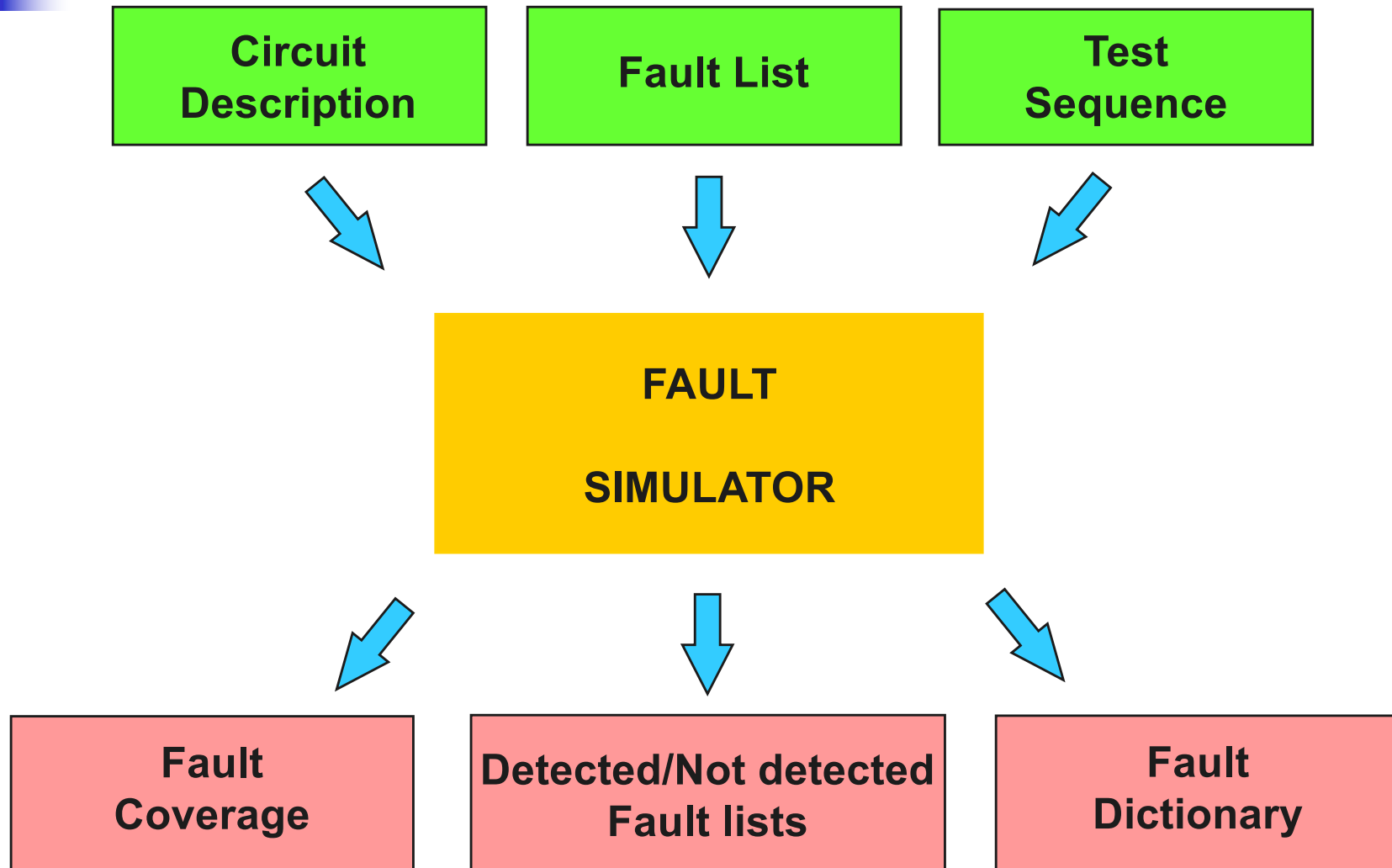



Constraints

- Circuit description
 - Functional, structural
- Fault models
 - Stuck-at, bridging, delay ...
- Coding
 - Two values (0,1)
 - Three values (0, 1, X)
 - Four values (0, 1, X, Z)



Constraints

- Timing

- Zero-delay → No delay considered during the simulation
- Unit-delay → A delay is associated to each gate



Fault Simulation Techniques

- Serial fault simulation
- Parallel fault simulation
- Deductive fault simulation
- Concurrent fault simulation




Serial Fault Simulation

- A golden circuit simulation + n independent simulations of the n faulty circuits (for n considered fault)
- Pros:
 - Simple. Does not require the development of a specialized fault simulator. Can be implemented from a classic logic simulator.
 - Able to simulate any type of fault that can be taken into account by the logic simulator.
 - Low memory space requirement
- Cons:
 - Very slow ($n+1$ consecutive simulations for a list of n faults)

 Exercise

- Determine the faults detected by the vectors:
 $V(a,b) = (1,1)$ et $(0,0)$






Parallel Fault Simulation

- Principle

- Takes advantage of parallel (per-word) processing of binary information in computers
 - If the host computer manipulates n-bit words, the golden circuit and the n-1 faulty circuits can be simulated in parallel
 - ⇒ The number of faults considered during a simulation depends on the length of the computer words
 - ⇒ Fault simulation performed in some phases
- Each circuit net is associated with a n-bit words
 - The first bit represents the logic state of the golden circuit
 - Each other bit represents the state of a faulty circuit

Example

 




Methodology

- Faults are taken into account (or injected) via logic masks
 - A Sa1 at net E is injected by “ORing” the word of E and the Sa1_mask
 - A Sa0 at net E is injected by “ANDing” the word of E and the Sa0_mask

Sa0 and Sa1 Masks

 - Fault injection masks are taken into account when evaluating the output of a gate







AND Gate Example

- ma and mb are the two words assigned to the AND gate inputs (a, b)
- $p0$ and $p1$ are the two masks corresponding to Sa0 and Sa1 faults on output c of the AND gate
- Computation of word mc (output of the AND gate)
 - $mc = ma \cdot mb$ for the golden gate
 - $mc = ma \cdot mb \cdot p0$ if the Sa0 on c is considered only
 - $mc = ma \cdot mb + p1$ if the Sa1 on c is considered only
 - $mc = ma \cdot mb \cdot p0 + p1$ if both SaF are considered

General Case

 

Example (1)

 

- A 5-bit word

Golden	S1 Sa0	S1 Sa1	S2 Sa0	S2 Sa1
--------	--------	--------	--------	--------



Example (2)

- Masks

- $s1 \text{ Sa0 } p0(s1) = 10111$ $s2 \text{ Sa0 } p0(s2) = 11101$
- $s1 \text{ Sa1 } p1(s1) = 00100$ $s2 \text{ Sa1 } p1(s2) = 00001$

- Test vector

- $V(e1, e2, e3) = 110$
 $m(e1) = 11111, m(e2) = 11111$ et $m(e3) = 00000$

- Parallel fault simulation

- $m(s1) = m(e1) \cdot m(e2) \cdot p0(s1) + p1(s1) = 10111$
- $m(s2) = (m(s1) + m(e3)) \cdot p0(s2) + p1(s2) = 10101$



Example (2)

- Masks
 - $s1$ Sa0 $p0(s1) = 10111$ $s2$ Sa0 $p0(s2) = 11101$
 - $s1$ Sa1 $p1(s1) = 00100$ $s2$ Sa1 $p1(s2) = 00001$
- Test vector
 - $V(e1, e2, e3) = 110$
 $m(e1) = 11111, m(e2) = 11111$ et $m(e3) = 00000$
- Parallel fault simulation
 - $m(s1) = m(e1) \cdot m(e2) \cdot p0(s1) + p1(s1) = 10111$
 - $m(s2) = (m(s1) + m(e3)) \cdot p0(s2) + p1(s2) = 10101$
- Fault simulation result
 - Golden circuit response $\rightarrow s2 = 1$
 - $V = 110$ detects Sa0 faults on $s1$ et $s2$



Exercise

- Test vector $\rightarrow V(a,b) = (1,1)$

