



Chapter 7

Design-for-Test

Arnaud Virazel

virazel@lirmm.fr



Why?

- To ensure that a circuit (or system) is testable (technical and financial aspects)
- Test cost
 - Automatic Test Pattern Generation
 - Fault simulation
 - Tester (ATE), test equipment (investment)
 - Test time (effective time on the tester)



Objectives

- **Reduce** the time to market
 - by making the test vector production phase easier (or even automated)
- **Reduce** the test cost
 - by generating smaller test sets
- **Improve** the quality of the test
 - by increasing the fault coverage



DfT Techniques

- Ad-hoc techniques
 - common sense rules from experience
- Structured techniques
 - facilitate access to internal memorization points
 - standard for testing boards and systems
 - can be automated



Ad-hoc Techniques


- Initialization of memory points
- Logic partitioning
- Clock isolation
- Test point insertion
- Facilitate access to buses
- Make the circuits easily initializable
- Polarize the tri-state buses
- Avoid asynchronous circuits



Logic Partitioning


- CPU time for test pattern generation about G^n order (G number of gates and $2 < n < 3$)
- Divide and conquer approach
 - p partitions of G / p gates
 - Ex: original circuit with $G = 10000$
 - ⇒ CPU time: $G^2 = 10^8$
 - 2 partitions G_1 and G_2 of 5000 gates
 - ⇒ CPU time: $G_1^2 + G_2^2 = 5 \cdot 10^7$
 - ⇒ 2 times shorter
 - gain of p^{n-1} times ($p \times (G/p)^n$ compared to G^n)
 - partition into logically independent parts

Logic Circuit Partitioning

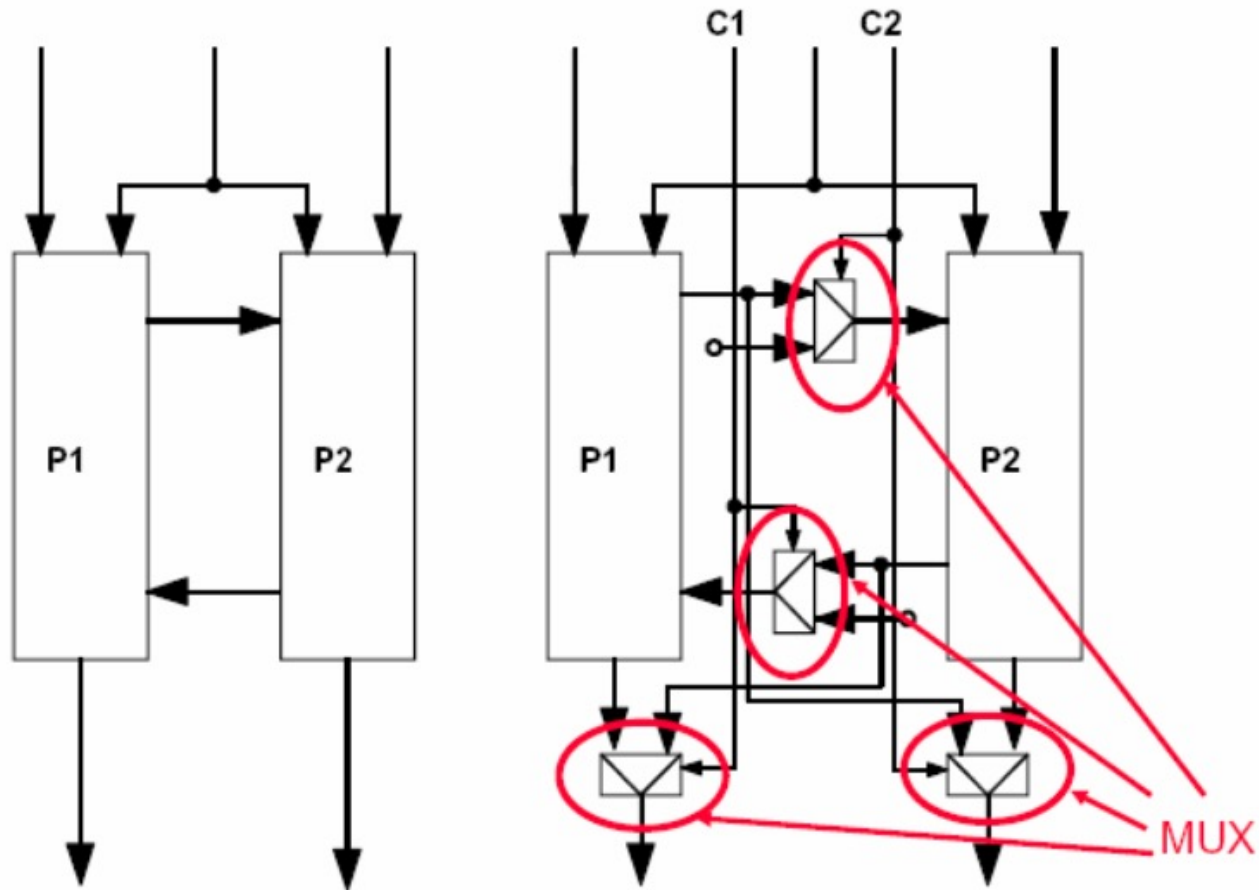


Clock Isolation

■ Logic isolation

 


■ Hardware isolation

 


Critical Problem

 - CLK and data generated by the same signal
- Sequencing is function of logics A and B delays (variability issue)
- Unpredictable results




Counter Bypass

 - Counters and frequency dividers increase sequential complexity
- Ineffective for ATPGs and testers
- Solution: multiplex the output with a signal that is easier to control by the ATE




Test Point Insertion

 
- Improved controllability and observability
 - reduction in the number of vectors
 - improved diagnosis
- Increase in the number of I / O
 - additional pads



Original Circuit

 

Control at 0
and Observability

 

Control at 0 and 1



Where to Inject?

- **Controllability**

- inputs of sub-circuits that are difficult to control
- initialization inputs of storage element
- control of three states
- Control of multiplexers
- enable and R / W of memories
- return loops

- **Observability**


- outputs of sub-circuits that are difficult to observe
- inaccessible control lines
- serial output of shift registers
- clock lines
- return loops




Scan Path

- Objectives
 - Make all flip-flops fully controllable and observable
 - Make the sequential circuit testing "equivalent" to combinational one

Sequential Circuit

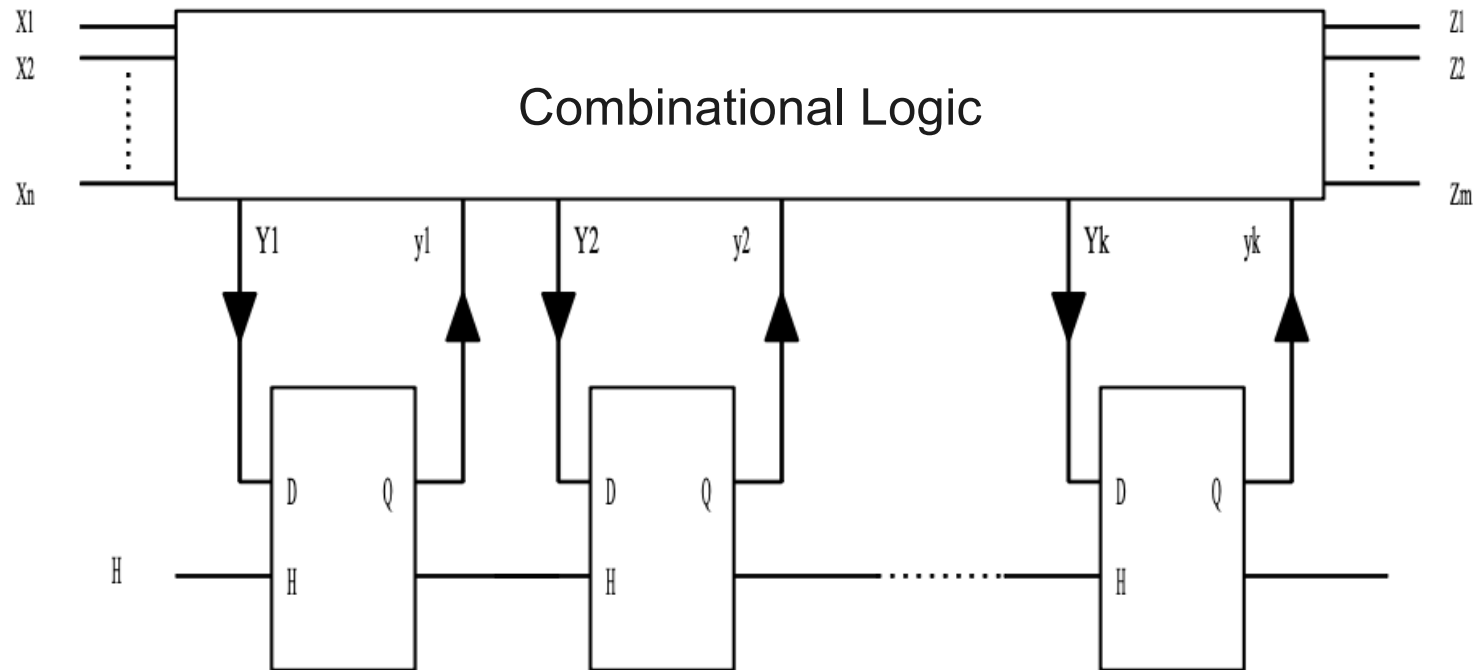

Scan Path Insertion

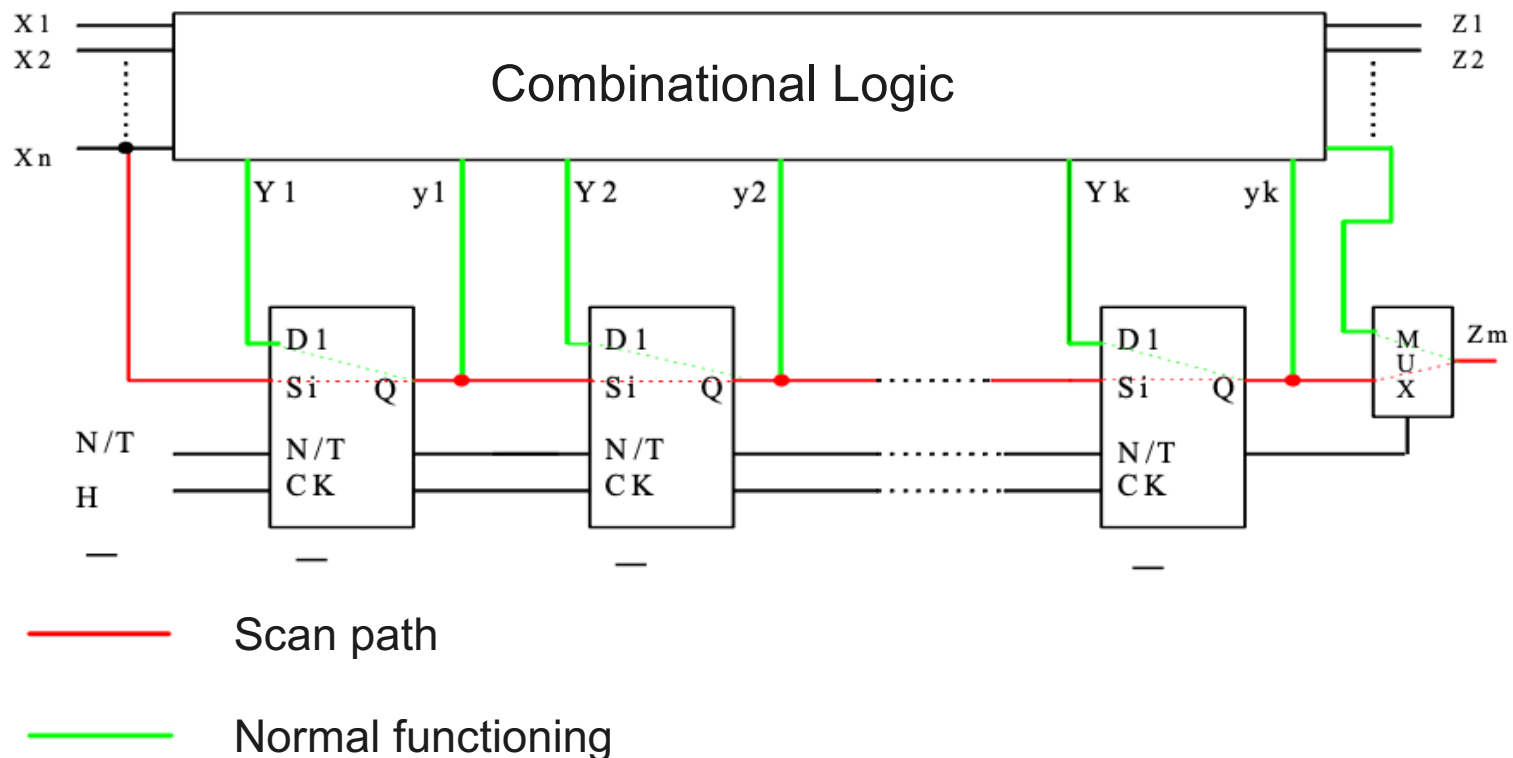


- Flip-flop modification (additional mux)
- Creation of a shift register (scan chain) allowing full observability and controllability of all storage nodes




Scan Test Procedure

- 0) Test of the scan chain (sequence of k times 01)
- 1) Place the circuit in test mode ($N / T = 1$)
- 2) Shift-in the test vector $\{y_1, \dots, y_k\}$ inside the scan path
- 3) Set the corresponding test values on the primary inputs X_i
- 4) Place the circuit in functional mode ($N / T = 0$) and after a time necessary for the stabilization of the outputs of the combinatorial part, check the different outputs Z_k
- 5) Apply a clock pulse to capture the test responses into the scan chain
- 6) Place the circuit in test mode ($N / T = 1$) and the contents of the shift register via the output Z_m and compare it with the expected results (shift-in at the same time the next test vector)

Waveform

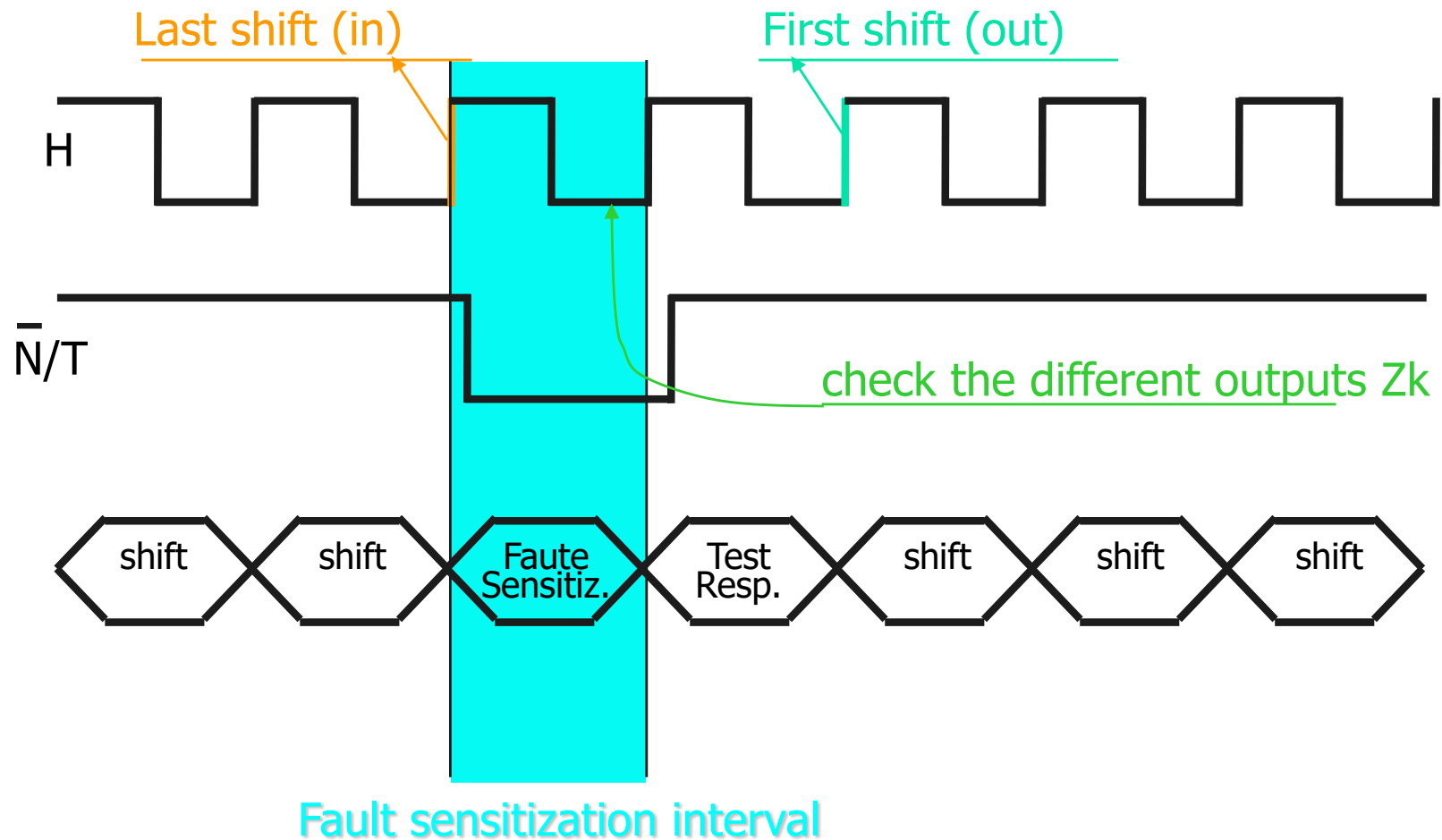

Example

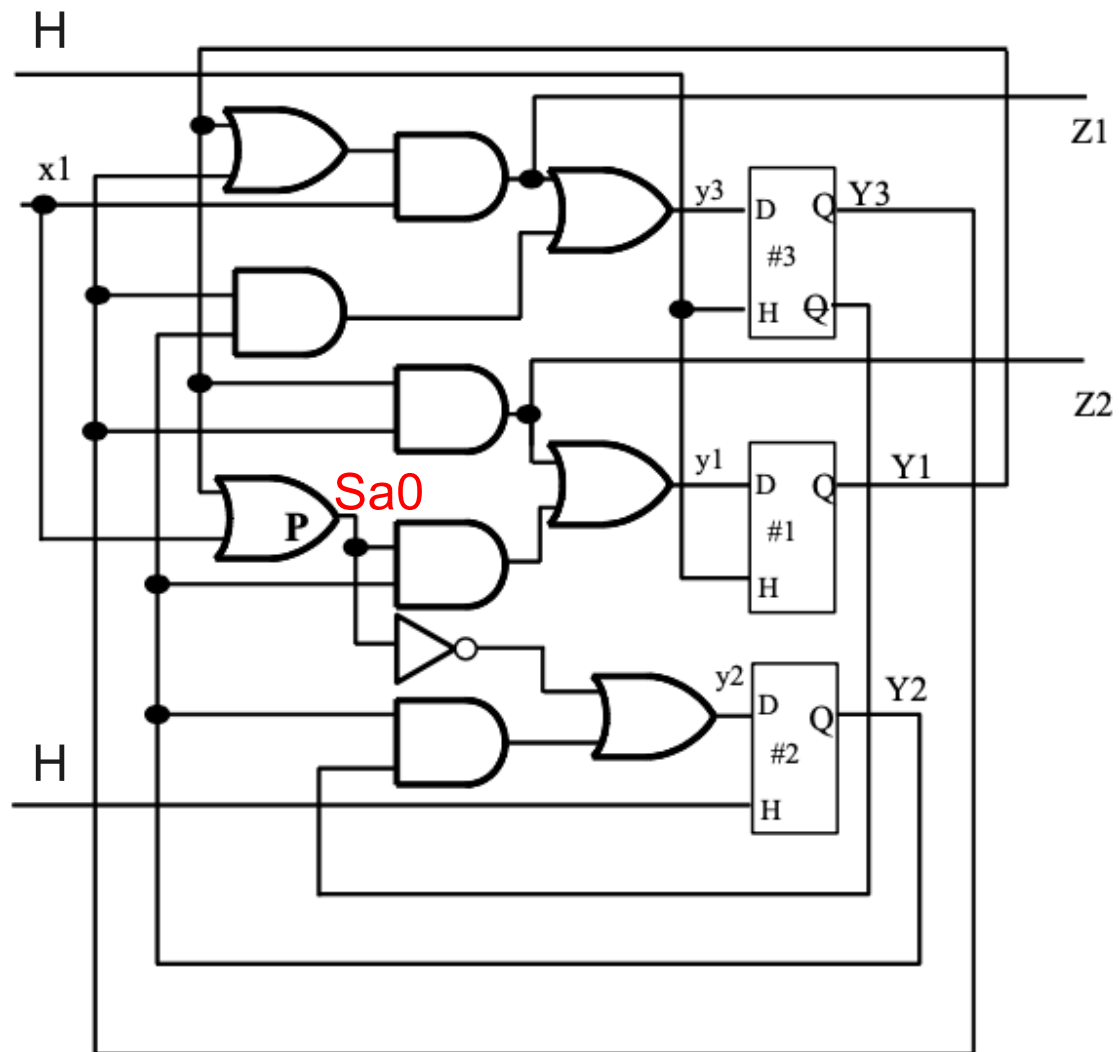




Drawbacks and Solutions

- Area overhead ("Scan" flip-flops, routing, pins)
- Degradation of the nominal operating speed (multiplexers)
- Test time duration of test time: $(nb\text{-test}) \times (nb\text{-FF})$




- Different Scan techniques
 - Multiple scan -> STUMP
 - Partial scan


Multiple Scan

 

 
- Single Scan chain
 - Reduce number of additional I/O
 - Long test time
 - ATE with a large memory depth



 
- Multiple Scan chain
 - Reduced test time
 - Reduced ATE memory depth
 - Improved diagnosis
 - Increase in the number of necessary I/O



STUMP Architecture

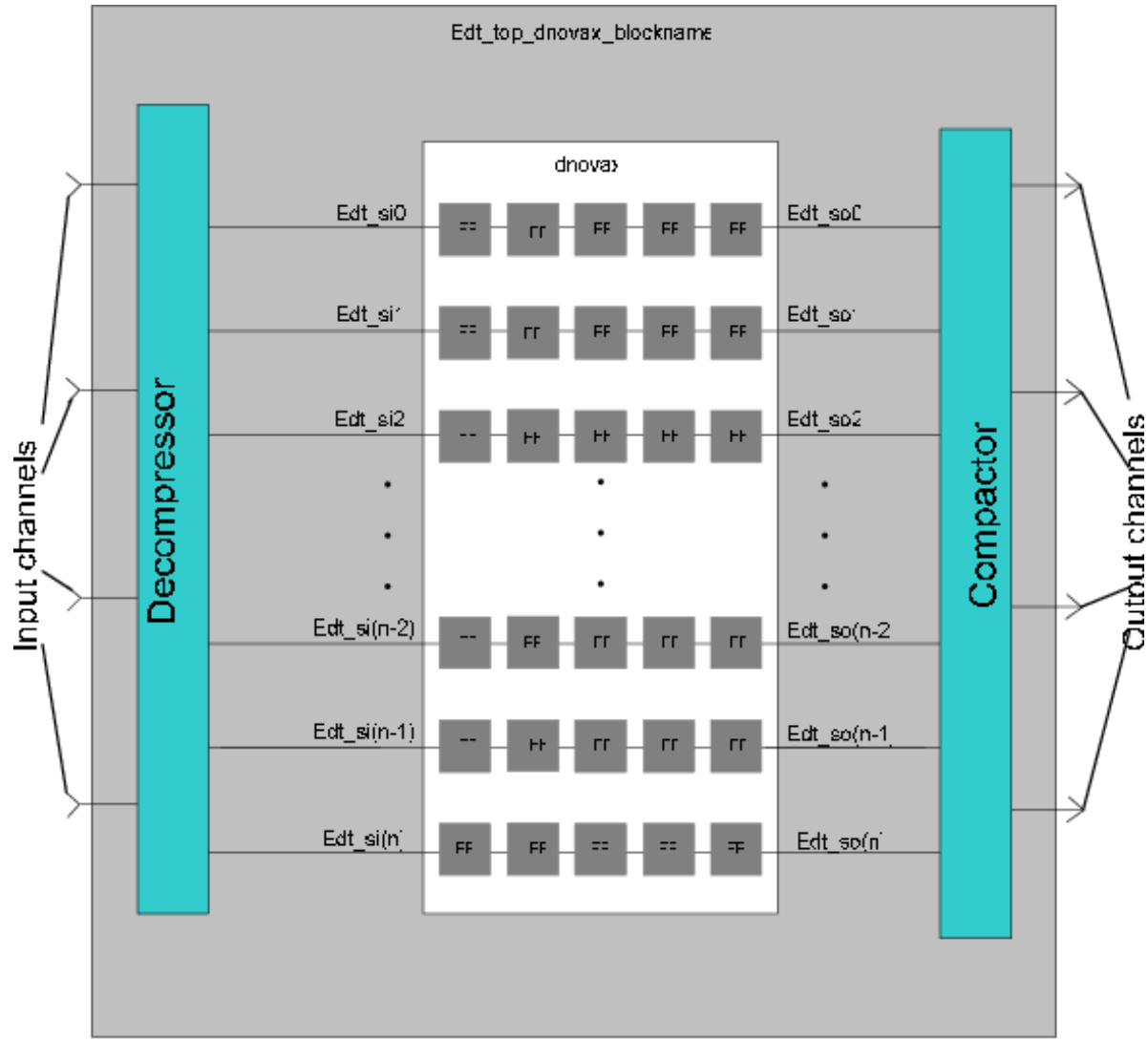

Partial Scan

 

- All memory elements are not included in the chain
- Require an ATPG for sequential circuit
- Problem of the "good choice" of flip-flops to include in the scan chain
- Less area footprint compared to full Scan
- Time performance improvement



Flip-Flop Selection

- Different approaches based on
 - the use of testability measures (less controllable/observable FFs are selected)
 - the generation of test vectors (propagation and justification phases)
 - the structural analysis (reduction of the depth of sequentiality and number of cycles)
 - a mixed use of these different techniques
- Consideration of constraints
 - critical path for example